

Beyond classical circuit design

lecture 10

Clocked Design &
Pipelining (Clocked & Asynchronous)


Further Reading

Jan M. Rabaey, Anantha Chandrakasan, Borivoje Nikolic: *Digital Integrated Circuits. A Design Perspective. 2nd edition.* Prentice Hall, 2003.



Ivan E. Sutherland: *Micropipelines.* Commun. ACM 32, 6 (June 1989), 720-738.

Steven M. Nowick, Montek Singh: *High-Performance Asynchronous Pipelines: An Overview.* Design & Test of Computers, IEEE , vol.28, no.5, pp.8,22, Sept.-Oct. 2011


Clocked Design

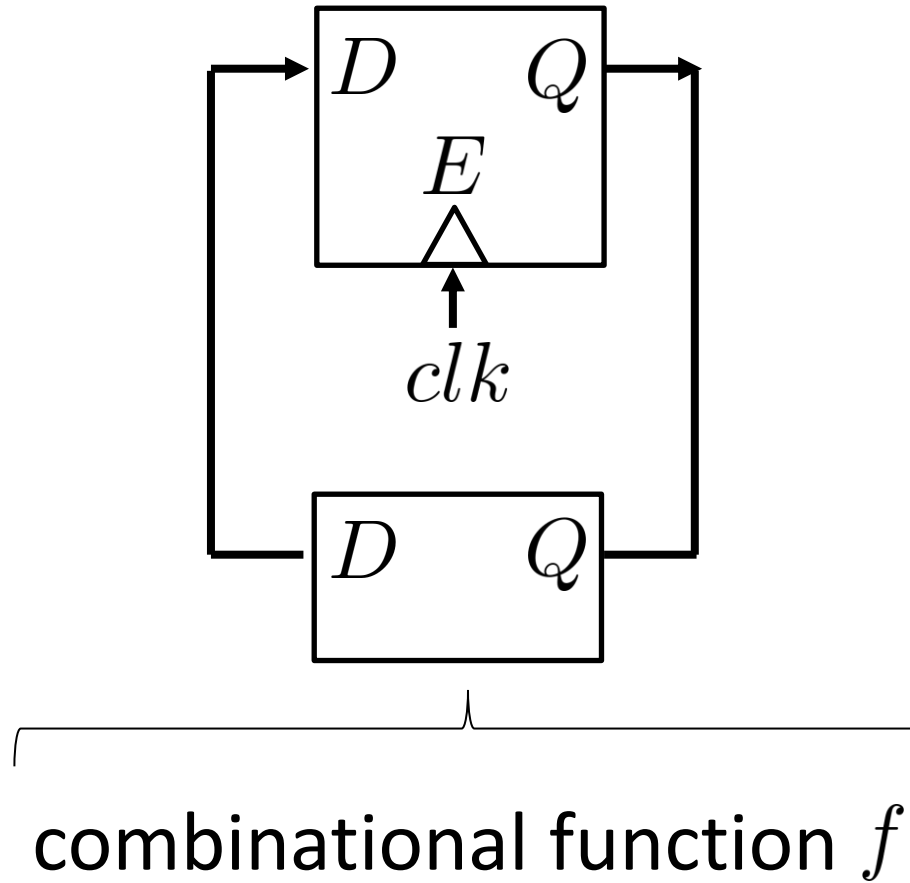


Clocked Design

 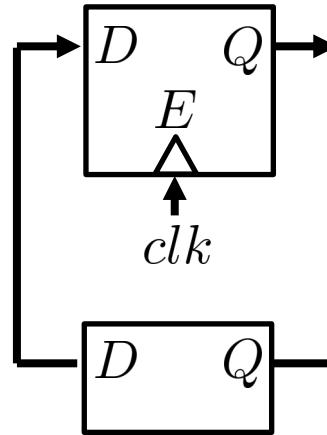

Clocked Design in Environment

 


next state logic

 

Moore machine



Variants

 

next state logic


Moore machine

Variants

 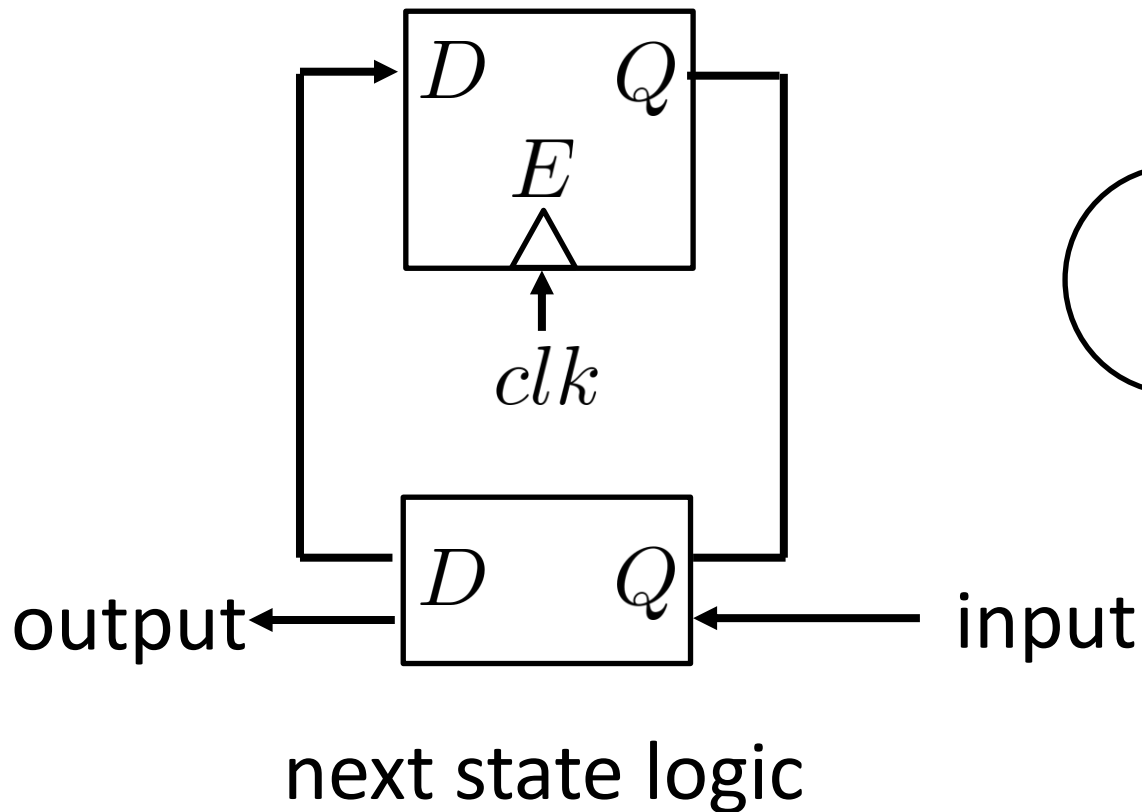


Mealy machine

Variants

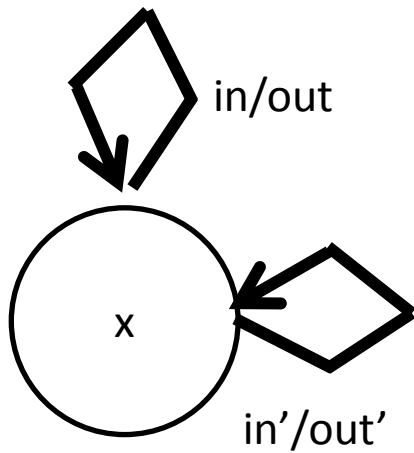

versus

 

Mealy -> Moore: split states per output

Beyond classical circuit design


lecture 10.5

Dynamic CMOS


Dynamic CMOS

Like in pseudo nMOS: remove slow pMOS stack.

But:

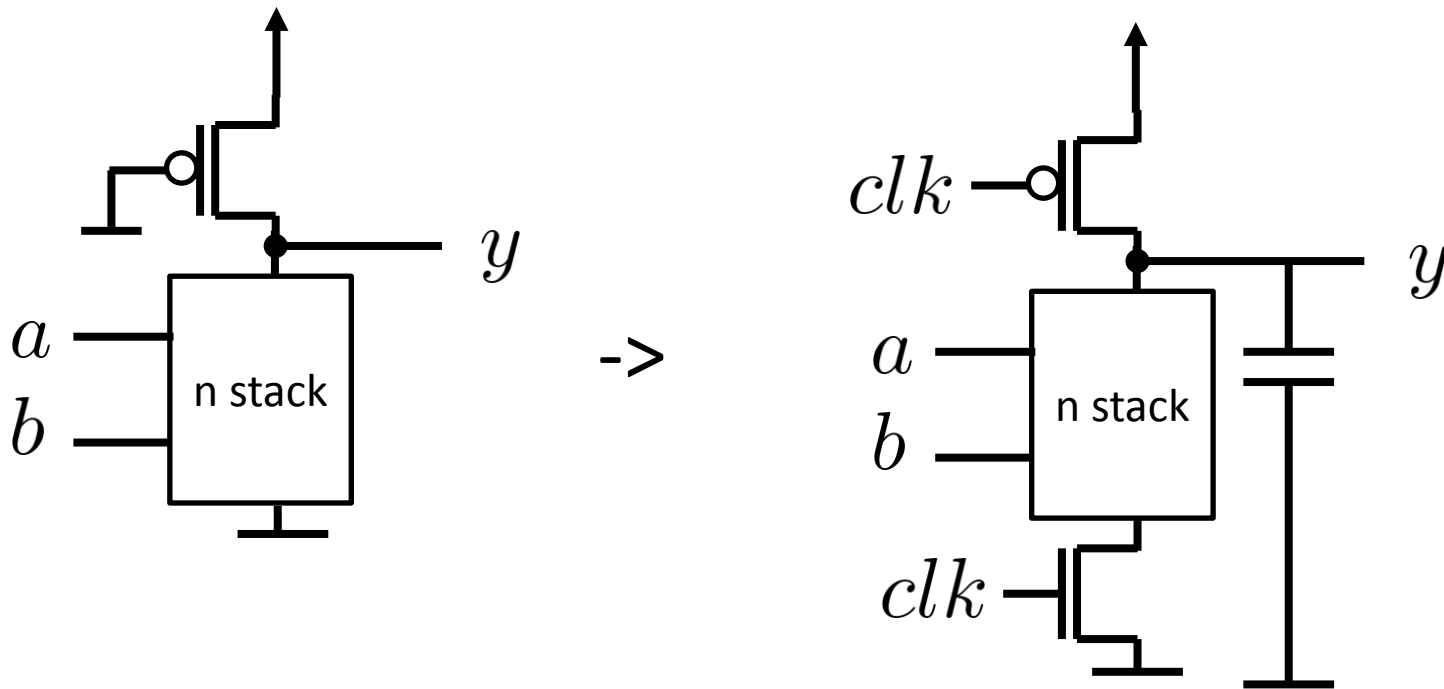


Dynamic CMOS 4NAND

 


Dynamic CMOS INV

 1. Precharge output & apply input (here 1)




Dynamic CMOS INV

2. Evaluate at active clock transition

 


Dynamic CMOS INV

 1. Precharge output & apply input (here 0)



Dynamic CMOS INV

2. Evaluate at active clock transition

 

Dynamic CMOS Properties

Glitches:

- + only transitions once from 1->0, or not at all

Speed:


- + very fast (only n stack & smaller load & 0 delay for 1 output)

Dynamic CMOS Properties

Power:


- + typically fewer transistors
- + only one transistor driven (n stack) instead of 2 (n stack and p stack)
- + only transitions once from 1- \rightarrow 0, or not at all
- potentially higher switching rate (!)
- clock transistor always switches

Charge Sharing

 


Charge Sharing

1. evaluate

 


2. next charging

 


Charge Sharing


3. evaluate

 

3'. at end of evaluation

 


Charge Sharing Workaround

 


Charge Sharing Workaround

1. evaluate

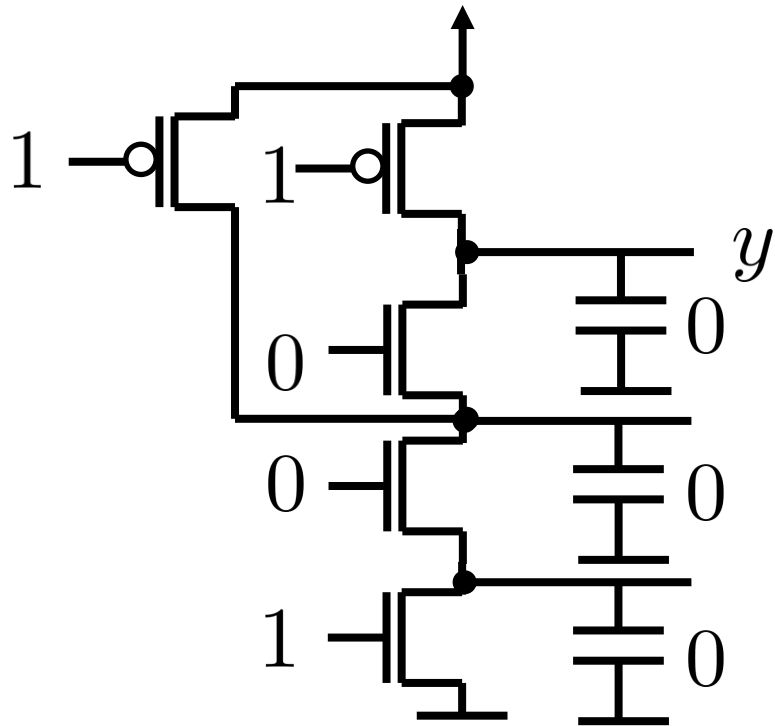


2. next charging

 


Charge Sharing Workaround


3. evaluate

 



3'. at end of evaluation

 


Cascading Gates

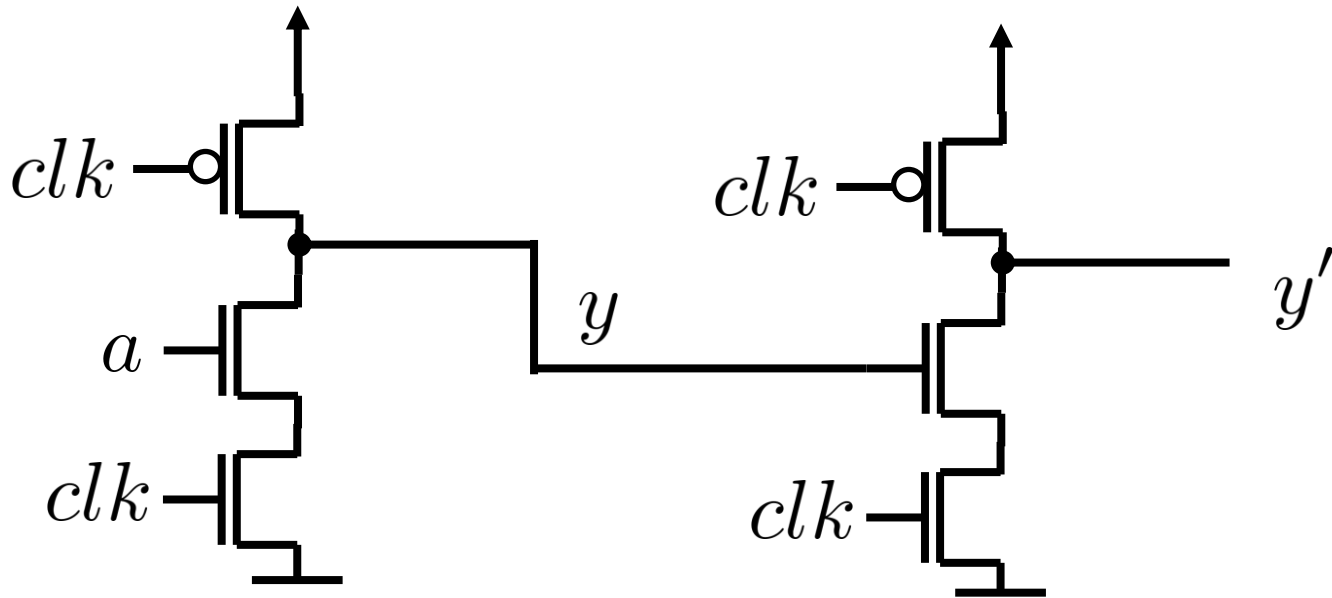

Cascading Gates

 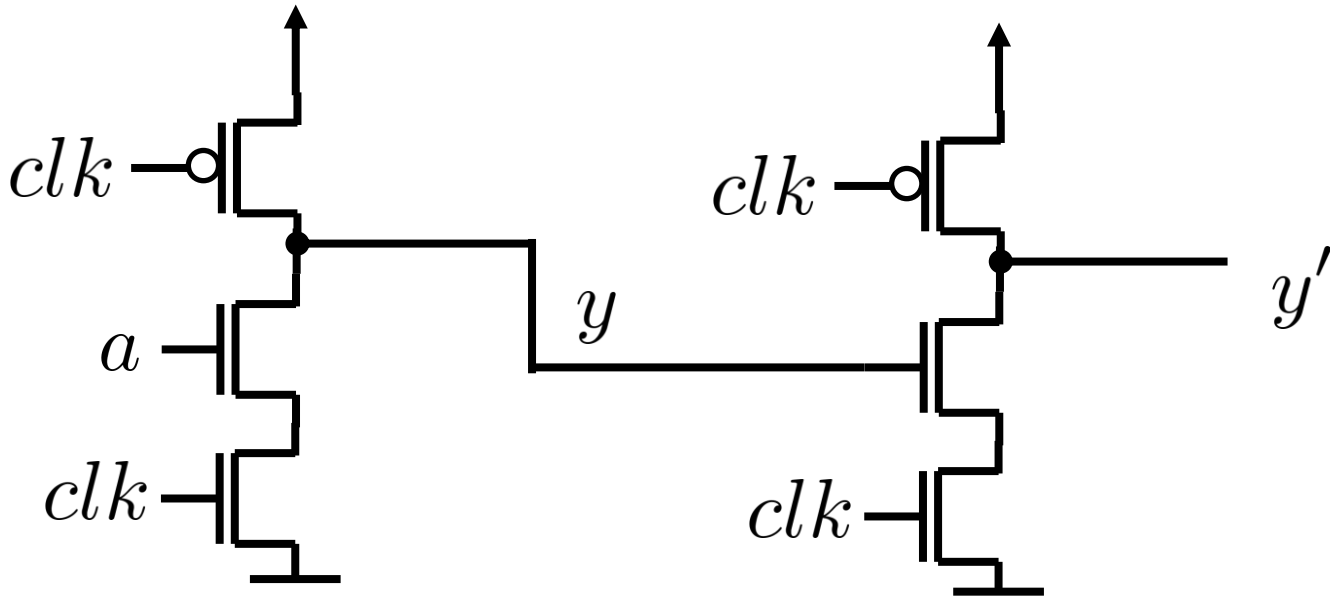

Cascading Gates: Domino Logic

 

Beyond classical circuit design


lecture 10.75

Pipelining


Pipelining

- In clocked/synchronous designs
- In clockless/asynchronous designs
 - static logic
 - dynamic logic


Synchronous Pipelining

 


versus

 

Balancing

 


versus

 


Clockless Pipelining

... with static logic

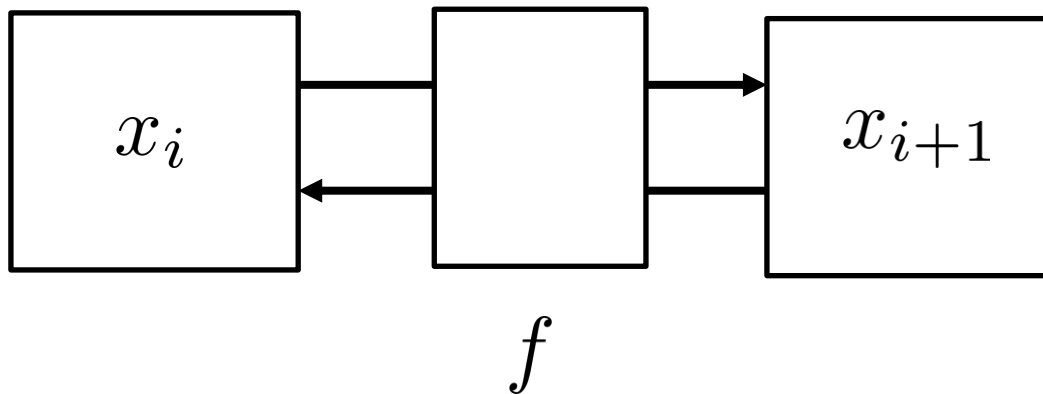Local handshaking instead of global clock




Capture-pass latch

 

$C = P \rightarrow$ pass D to Q

$C \neq P \rightarrow$ hold Q


Sutherland's Micropipeline

 


Sutherland's Micropipeline

- 2-phase handshaking (here)
- Bundled data (here)
- Initially all latches transparent (= pass mode)
- Constraints:
 - delays from C to Cp and from P to Pd need to be long enough for latch hold times
 - bundled data constraint


Control structure

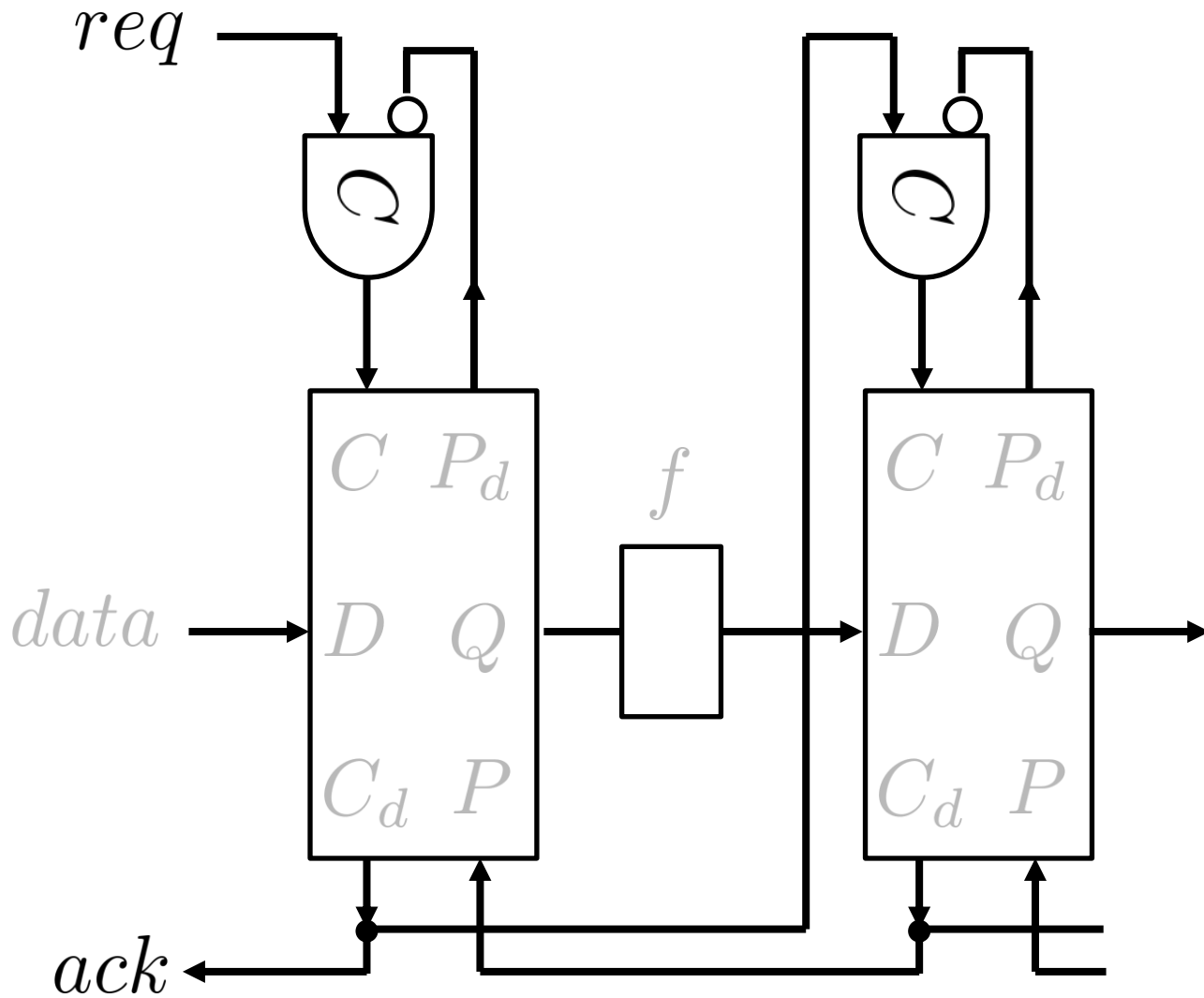


Control structure

 


Control structure

 


Control structure

 


Control structure

 


Control structure

 

Control structure

 


Control structure

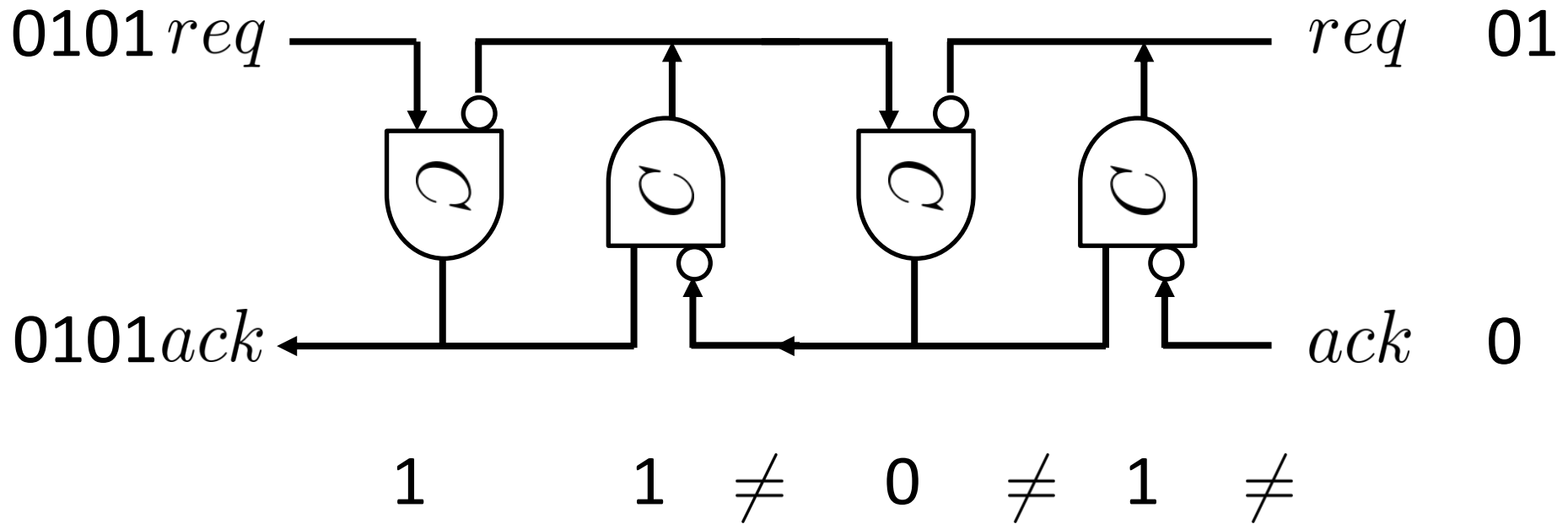

3 different consecutive C-states -> 3 "items" stored

Mousetrap pipeline

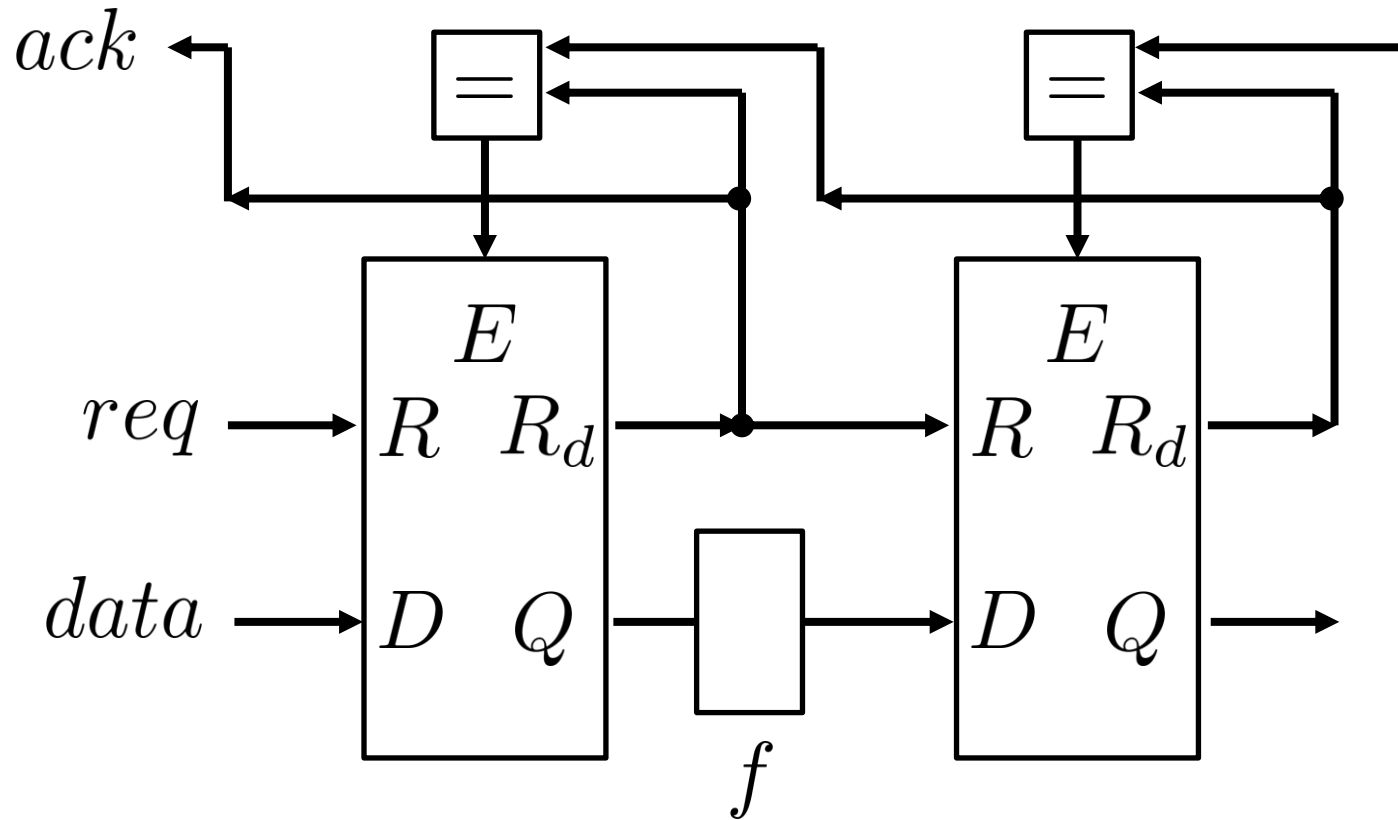


Mousetrap pipeline

- 2-phase handshaking
- Bundled data
- Initially all latches transparent (= pass mode)
- Constraints:
 - ack delay needs to be long enough for latch hold time
 - bundled data constraint

Clockless Pipelining


... with dynamic logic

Completion dedection

 

*[$v(data)$; $out \uparrow$; $n(data)$; $out \downarrow$]


Dynamic function block

 


$eval = 0 \rightarrow$ evaluate $out = f(data)$

$eval = 1 \rightarrow$ precharge *out* (here to all 0)


PSO pipeline

 


PSO pipeline

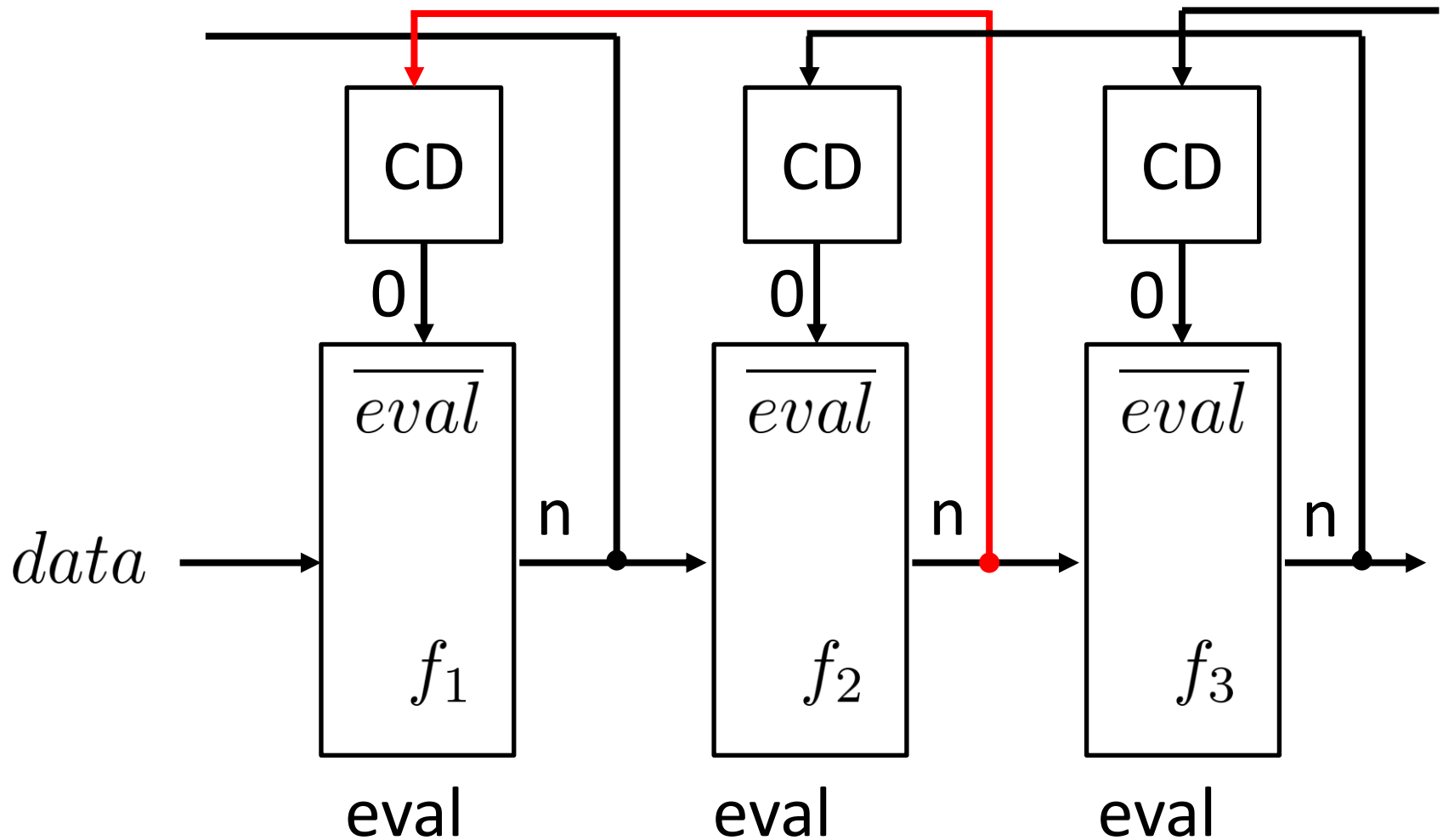

PSO pipeline

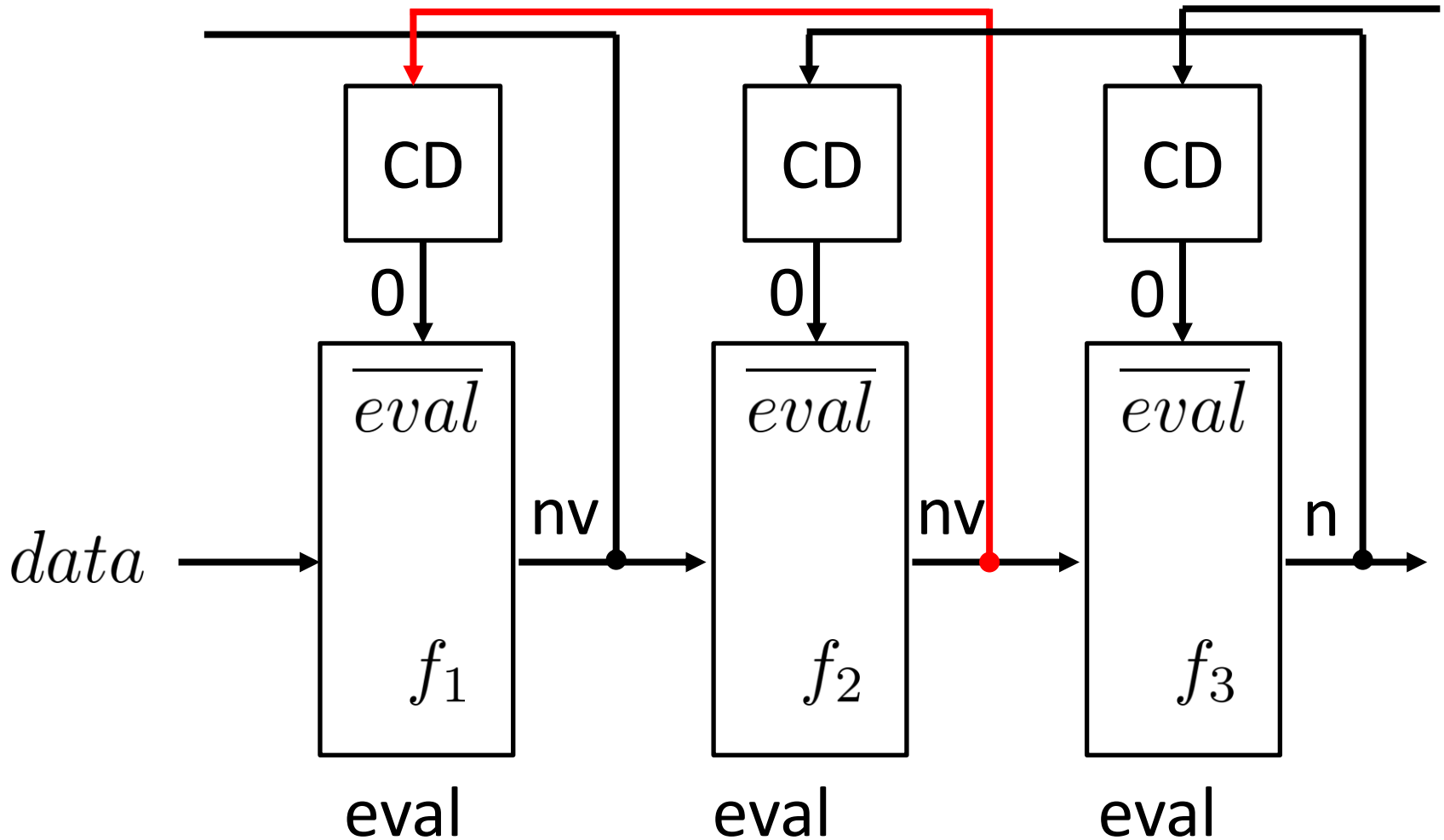


PSO pipeline

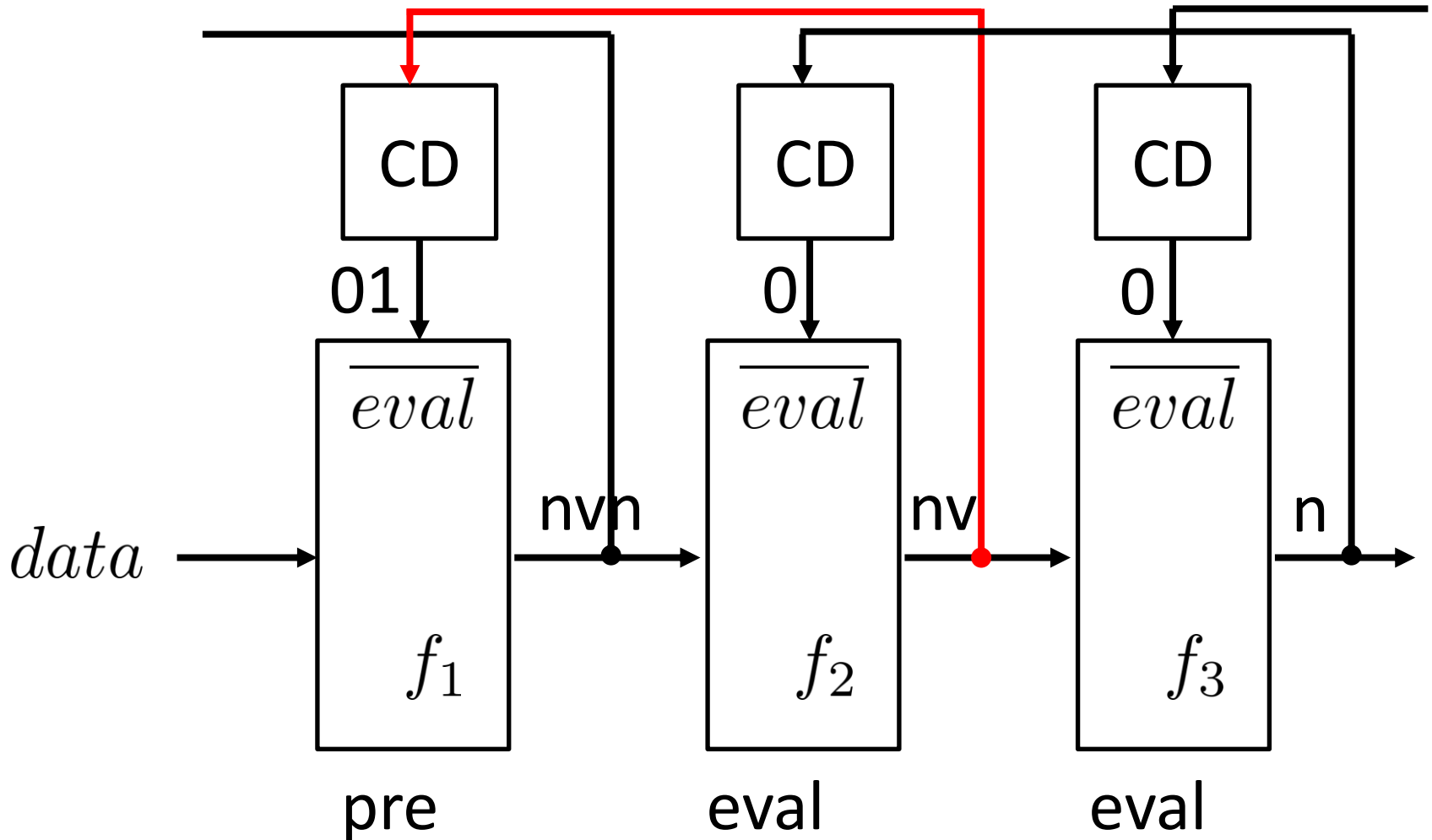


PSO pipeline

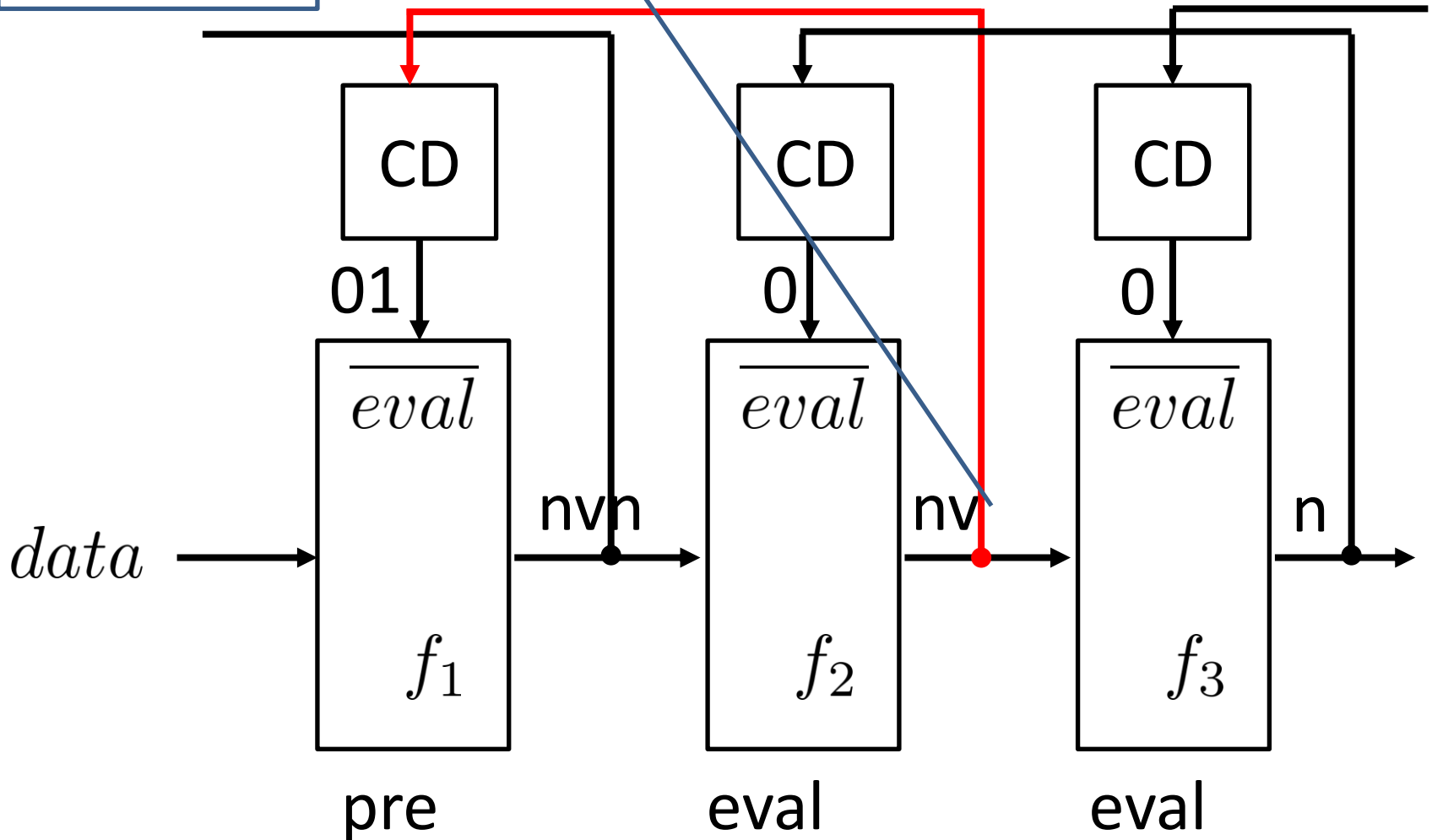
do not fall back
to n since
dynamic logic!




PSO pipeline

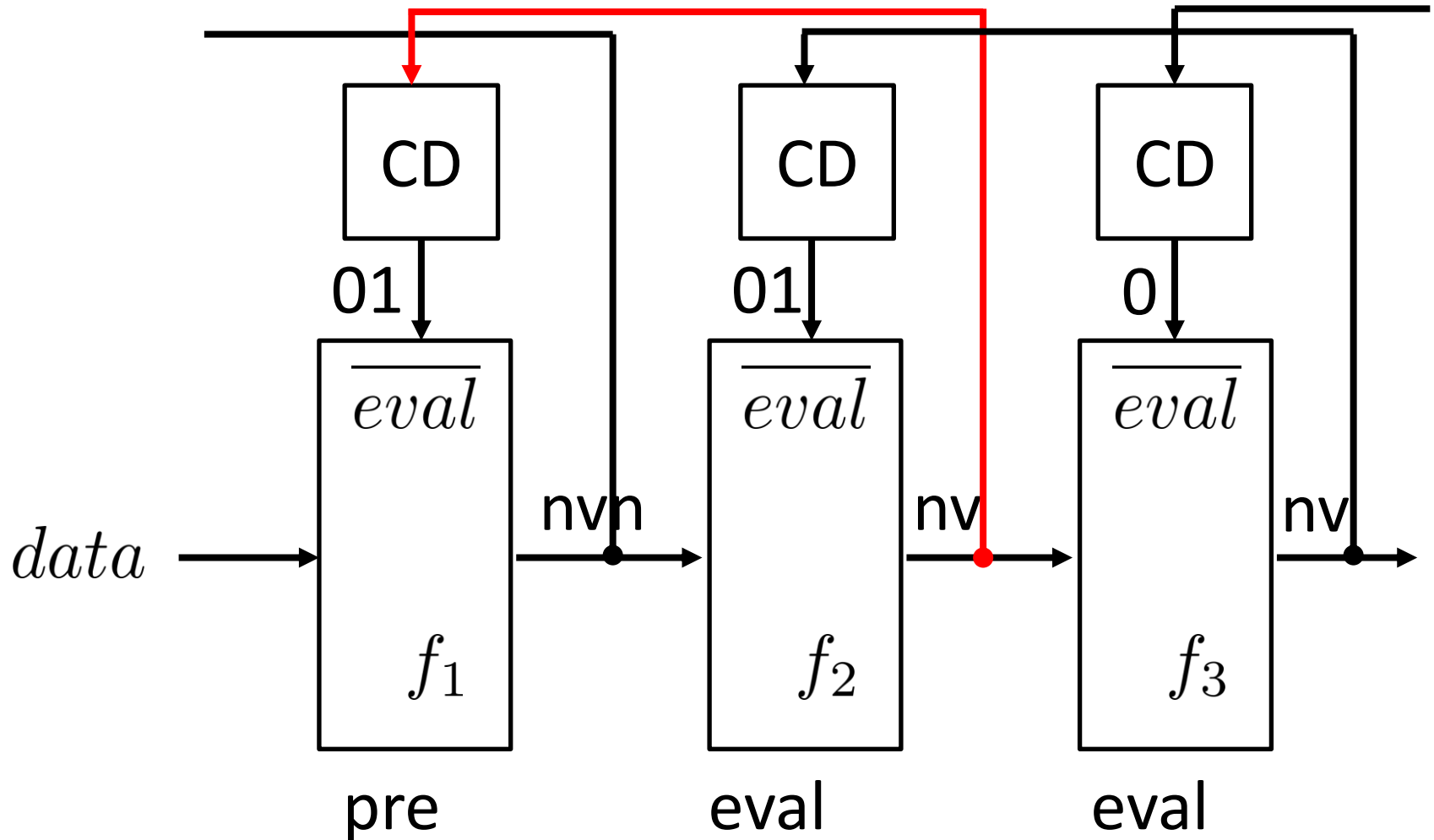

PSO pipeline

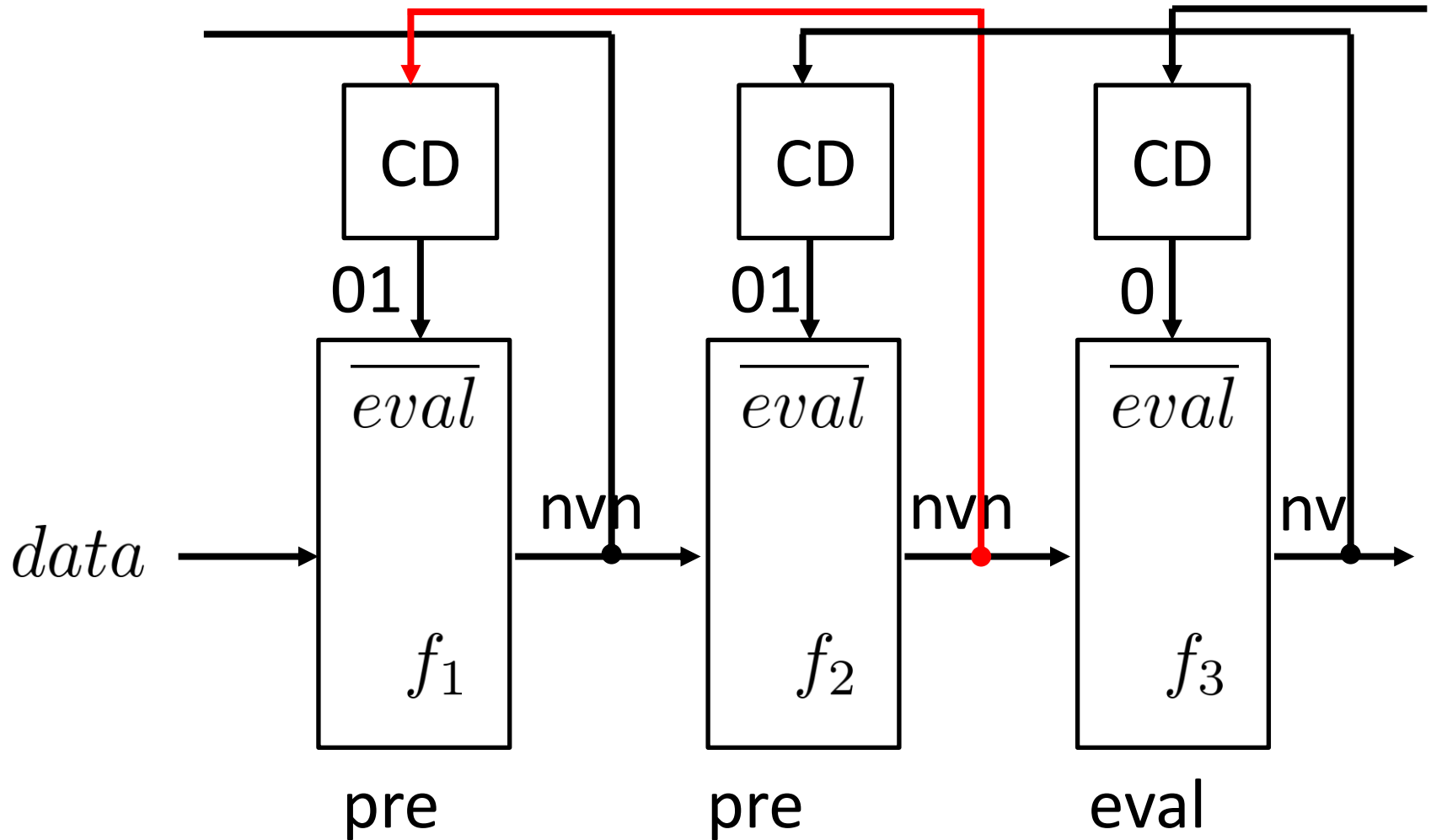


PSO pipeline

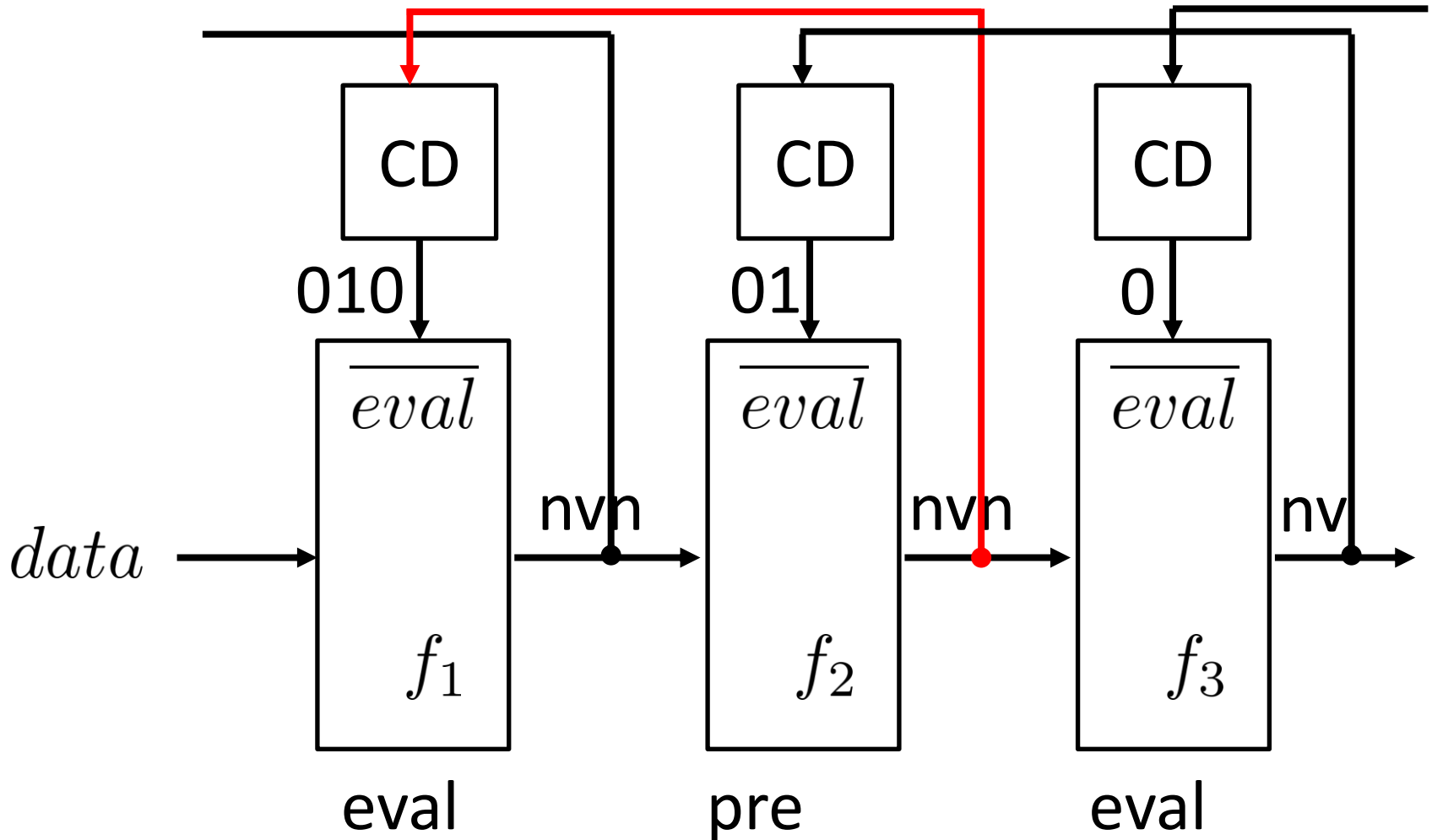

precharge
"spacer"
between two
data items

PSO pipeline

 

PS0 pipeline

- DI encoded data (here)
- Initially all latches transparent (= pass mode)
- Constraint:
 - CD delay needs to be long enough for latch hold time

PS0 pipeline

- + pros of dynamic logic
- handshake delays between 3 stages for “freeing” storage again after data wave
- spacers between data items
 - > can use only half the pipeline

Clockless pipelines

- + balancing not necessary (although can improve)
- + automatic “clock gating” (low energy)
- + very fast initial wave

Other static/dynamic pipeline designs exist that improve shown designs.