

Beyond classical chip design


lecture 3

Self-stabilization (continued)

What we had...

Distributed, weak-fair scheduler ->

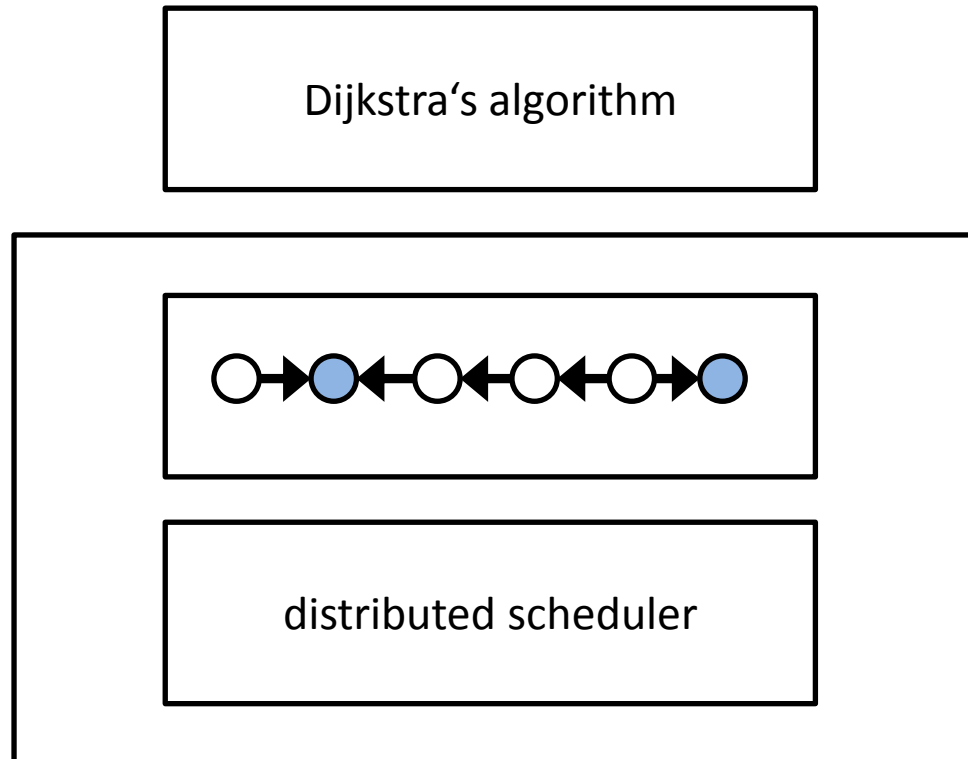Distributed, **neighbour-mutex**, weak fair scheduler.



Self-stabilization

... link reversal almost solves the problem.


token merging

LR

distributed schedule




Self-stabilization

stable algorithm

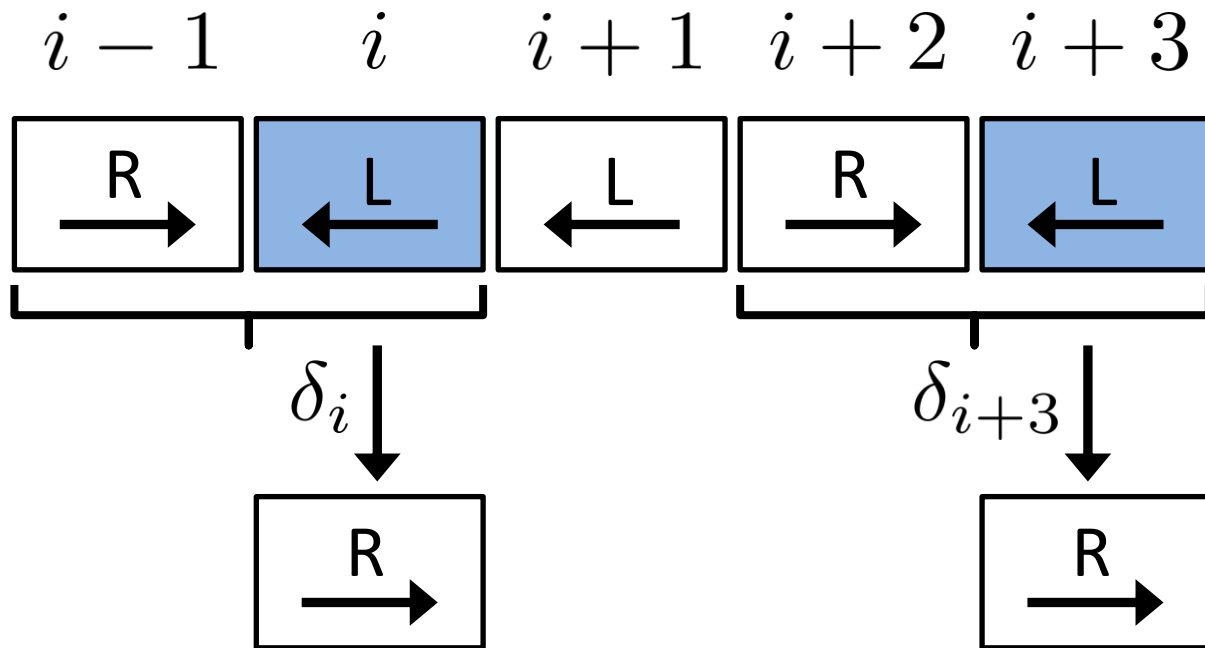

Self-stabilization

adding direction

   

Self-stabilization


tokens turn only at borders ->

Prop 1. Mutex holds.

Prop 2. Weak fairness holds.


Self-stabilization

to left ...

 


Self-stabilization

to right ...

 


... well

Self-stabilization

 


requires simultaneity: two sided constraint!

Self-stabilization

 


... one sided

Self-stabilization

 


... without timing?

Self-stabilization

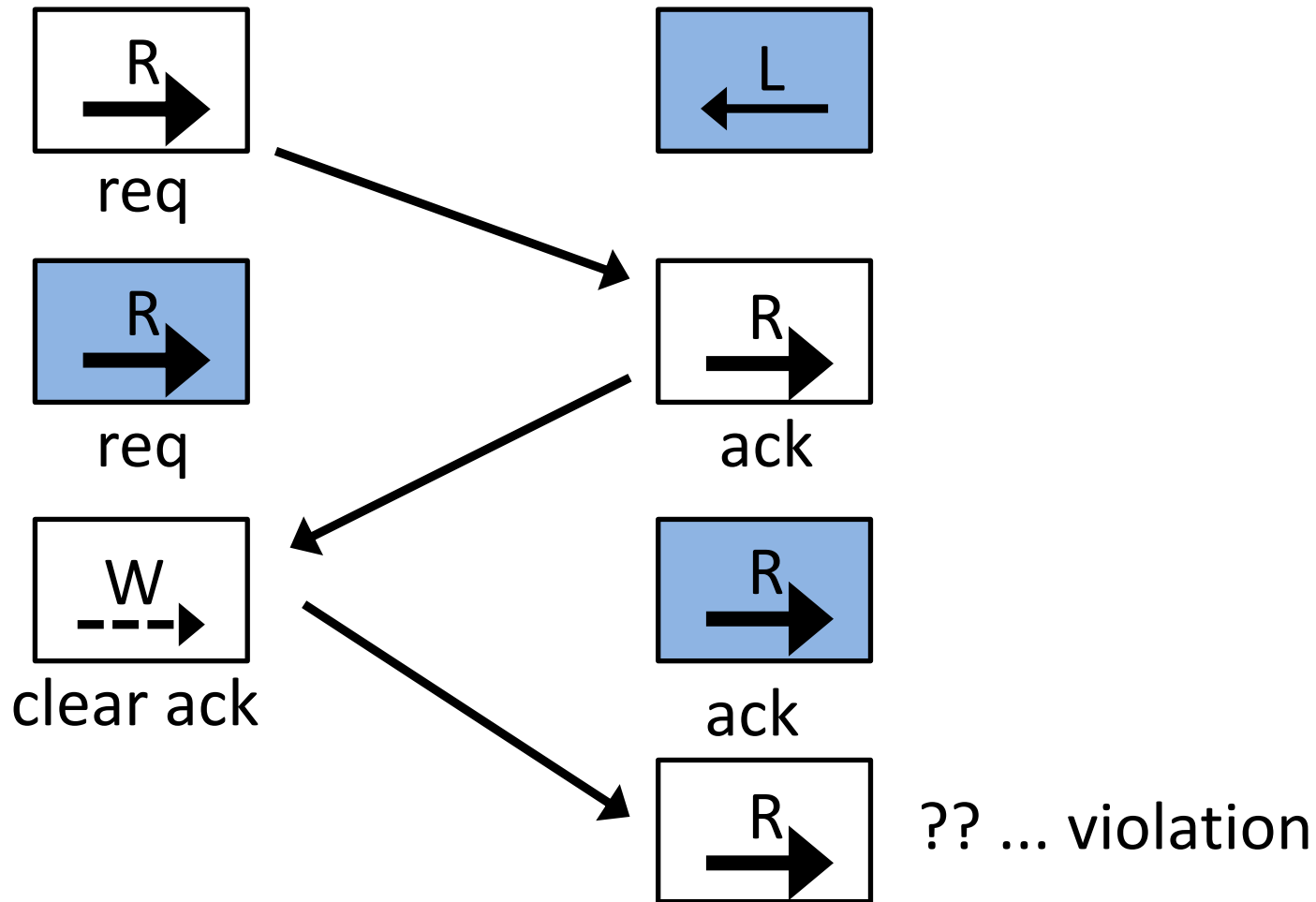

Self-stabilization

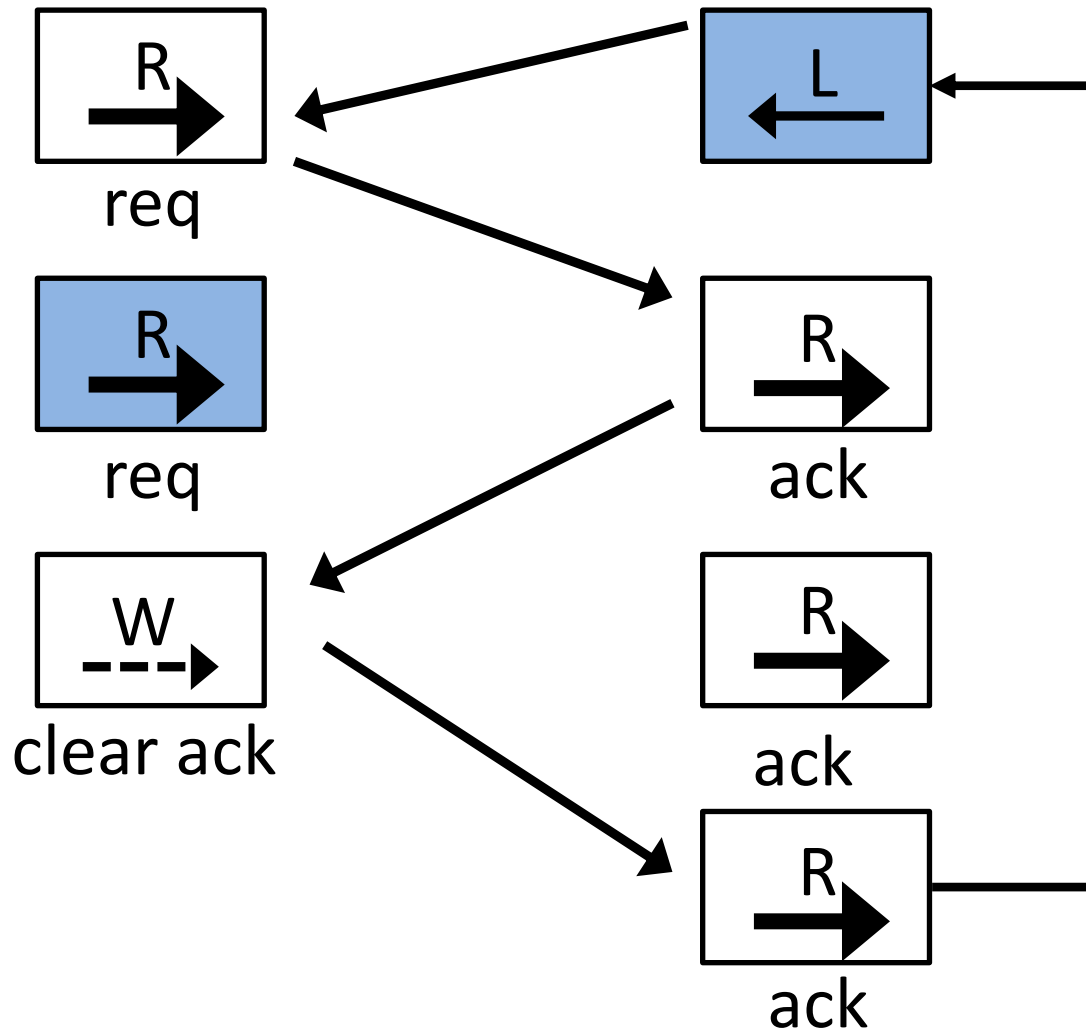

Beyond classical circuit design

lecture 3.5

Circuit model

Further Reading

Alain J. Martin: *Synthesis of Asynchronous VLSI Circuits*. Tech report California Institute of Technology, 1991.

Alain J. Martin and Mika Nyström: *Asynchronous techniques for system-on-chip design*. Proceedings of the IEEE Volume 94, Issue 6:1089 - 1120, June 2006.

Binary, event based model

here [Alain Martin]:

low-level: production rules.

high-level: communicating hardware processes.

Low-level Specifications

Production rules

Production rules

variable/port: from a finite alphabet V

transition: variable + up/down

production rule: Boolean guard \rightarrow transition

$$x \wedge y \rightarrow z \uparrow$$

$$\neg(x \wedge y) \rightarrow z \downarrow$$

Production rules

$$x \wedge y \rightarrow z \uparrow$$

$$\neg(x \wedge y) \rightarrow z \downarrow$$

typically rule-pairs

non-interference: per rule-pair $\neg(Bu \wedge Bd)$


no self-reference: per rule

Gate

gate = rule-pair

combinational (NOT, 2AND, 2OR, AOIs, ...)

$$Bu \leftrightarrow \neg Bd$$

 

$$x \wedge y \rightarrow z \uparrow$$

$$\neg(x \wedge y) \rightarrow z \downarrow$$

Gate


gate = rule-pair

state holding

set-reset latch

$$s \rightarrow z \uparrow$$


$$r \rightarrow z \downarrow$$

 

2C-Element


$$x \wedge y \rightarrow z \uparrow$$
 
$$\neg x \wedge \neg y \rightarrow z \downarrow$$



Wire

= special gate

 

$$i \rightarrow o \uparrow$$

$$\neg i \rightarrow o \downarrow$$

Production rules


circuit = algorithm = set of production rules

$$Au : x \wedge y \rightarrow z \uparrow$$

$$Ad : \neg(x \wedge y) \rightarrow z \downarrow$$

$$Du : i \rightarrow x \uparrow$$

$$Dd : \neg i \rightarrow x \downarrow$$

 

environment = set of production rules

Execution

global state $s : V \mapsto \{0, 1\}$

enabled rule, step

execution $(s_n)_{n \geq 0}$

constraints: (weak) fairness, partial order, timed

Hardware design



Given basic building blocks, implement the specification.

Circuit A implements circuit B

observable variables \mathcal{O}

trace inclusion
  
$$E_A \upharpoonright \mathcal{O} \subseteq E_B \upharpoonright \mathcal{O}$$





Circuit A implements circuit B

$i \uparrow x \uparrow i \downarrow y \uparrow z \uparrow \mapsto$


$i \uparrow i \downarrow y \uparrow z \uparrow$

-> A does not implement B

  


Mind...

wire + wire “is” not a (long) wire

 

 
$i \uparrow, x \uparrow, i \downarrow, y \uparrow, x \downarrow, y \downarrow$




Mind...

wire + wire “is” not a (long) wire

->

 

vs.

 


oscillations?! [hw]


“implements”

Simulation.

A:

 

B:

 


$i \uparrow$

“implements”


Simulation.

A:

 

$i \uparrow$

B:

 


$i \uparrow$

“implements”


Simulation.

A:

 

$i \uparrow$

B:

 


$i \uparrow i \downarrow$

“implements”


Simulation.

A:

 

$i \uparrow$ $i \downarrow$

B:

 


$i \uparrow$ $i \downarrow$

“implements”


Simulation.

A:

 

$i \uparrow i \downarrow$

B:

 


$i \uparrow i \downarrow y \uparrow$

“implements”


Simulation.

A:

 

$i \uparrow i \downarrow y \uparrow$

B:

 


$i \uparrow i \downarrow y \uparrow$

“implements”


Simulation.

A:

 

$i \uparrow i \downarrow y \uparrow$

B:

 


$i \uparrow i \downarrow y \uparrow i \uparrow$

“implements”


Simulation.

A:

 

$i \uparrow i \downarrow y \uparrow i \uparrow$

B:

 


$i \uparrow i \downarrow y \uparrow i \uparrow$

“implements”


Simulation.

A:

 

$i \uparrow i \downarrow y \uparrow i \uparrow$

B:

 


$i \uparrow i \downarrow y \uparrow i \uparrow z \uparrow$

“implements”


Simulation.

A:

 

$i \uparrow i \downarrow y \uparrow i \uparrow x \uparrow z \uparrow$

B:

 

$i \uparrow i \downarrow y \uparrow i \uparrow z \uparrow$

“implements”


A can simulate B.

Game rules:


- B makes a sequence of steps:
 - non-observables with ending observable
- A makes a sequence of steps:
 - non-observables with same ending observable

“implements”

 A can simulate B \rightarrow B implements A [hw]



 $i \uparrow i \downarrow y \uparrow i \uparrow x \uparrow z \uparrow$



$i \uparrow i \downarrow y \uparrow i \uparrow z \uparrow$

“implements”

A can simulate B \rightarrow B implements A [hw]

Simulation is an efficient test for implementation.

“implements”

A can simulate B \rightarrow B implements A [hw]

Simulation is an efficient test for implementation.

Is “can simulate” also necessary?

“implements”

A can simulate B \leftarrow B implements A ?

“implements”

$$\mathcal{O} = \{a, b, c, d\}$$


$$\top \rightarrow a \uparrow$$

$$[\perp \rightarrow a \downarrow]$$

$$a \rightarrow b \uparrow$$


$$b \wedge \neg d \rightarrow c \uparrow$$
 
$$b \wedge \neg c \rightarrow d \uparrow$$




“implements”

$$\mathcal{O} = \{a, b, c, d\}$$

 


“implements”

Circuit A

 

Circuit B

 


B implements A and A implements B.


A can simulate B

“implements”

Circuit A

 

Circuit B

 

B implements A and A implements B.
A can simulate B but B **cannot** simulate A.

“implements”

-> other notions of “can simulate”