

Beyond classical circuit design

lecture 6

Synthesis

Further Reading

Alain J. Martin: *Synthesis of Asynchronous VLSI Circuits*. Tech report California Institute of Technology, 1991.

Alain J. Martin and Mika Nyström: *Asynchronous techniques for system-on-chip design*. Proceedings of the IEEE Volume 94, Issue 6:1089 - 1120, June 2006.

Edmund M. Clarke, Orna Grumberg and Doron Peled: *Model Checking*. MIT Press, 1999.

What we had...

- Bare Handshakes -> Communication
- Isochronic fork assumption

- Coming up: Synthesis
 - CSP -> PR
 - PR -> transistors

Synthesis

In: CHP


Out: Circuit (= Production rules + constraints)

Example: 1-bit channel

Send $x \in \{0, 1\}$

active send,

passive receive

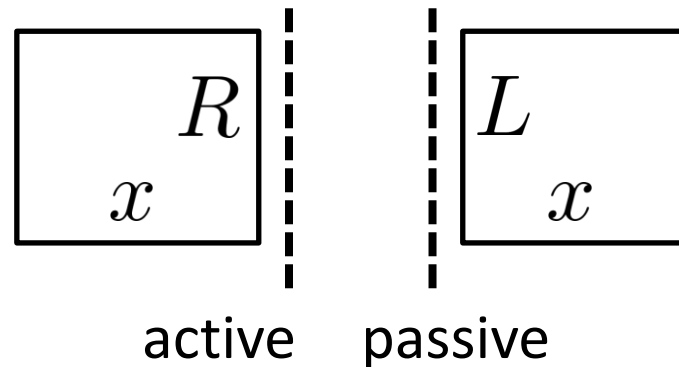

CHP:

sender: $P_s : *[\dots R!x \dots]$

receiver: $P_r : *[\dots L?x \dots]$

Example: 1-bit channel

Choice: dual-rail encoding.

$$R!x \quad rd := x; [v(ra)]; rd := neutral; [n(ra)]$$

$$[x \rightarrow rd.1 \uparrow \mid \bar{x} \rightarrow rd.0 \uparrow]; [ra];$$
$$(rd.1 \downarrow \mid rd.0 \downarrow); [\bar{ra}]$$

Example: 1-bit channel

$L?x \quad [v(ld)]; y := ld; la \uparrow; [n(ld)]; la \downarrow$



$[ld.1 \vee ld.0]; [ld.1 \rightarrow x \uparrow \parallel ld.0 \rightarrow x \downarrow]; la \uparrow;$
 $[\neg(ld.1 \vee ld.0)]; la \downarrow$




$[ld.1 \rightarrow x \uparrow \parallel ld.0 \rightarrow x \downarrow]; la \uparrow;$
 $[\neg(ld.1 \vee ld.0)]; la \downarrow$

Example: active-active sequencer

two active interfaces L, R.


CHP: $P1 : *[L; R]$

 



Example: active-active sequencer

two active interfaces L, R.

CHP: $P1 : *[L; R]$

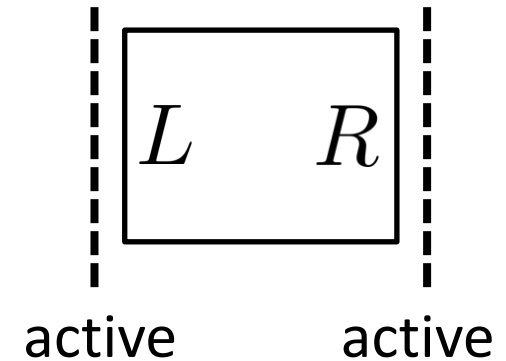


Choice: 4-ph hs

  

$*[lo \uparrow; [li]; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; ro \downarrow; [\bar{ri}]]$

For lo...

 

CHP: $*[lo \uparrow; [li]; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; ro \downarrow; [\bar{ri}]]$



$$lo = 0$$

by circuit

$$ro = 0$$




$$ri = 0$$

by environment

$$li = 0$$

For lo...

 

CHP: $*[lo \uparrow; [li]; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; ro \downarrow; [\bar{ri}]]$



$$lo = 0$$

by circuit

$$ro = 0$$




$$ri = 0$$

by environment

$$li = 0$$

PR: $\bar{lo} \wedge \bar{ro} \wedge \bar{ri} \wedge \bar{li} \rightarrow lo \uparrow$

For lo...

 

CHP: $*[lo \uparrow; [li]; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; ro \downarrow; [\bar{ri}]]$


$lo = 0$ $lo = 0$


$ro = 0$ $ro = 0$

$ri = 0$ $ri = 0$

$li = 0$ $li = 0$

 
PR: $\bar{lo} \wedge \bar{ro} \wedge \bar{ri} \wedge \bar{li} \rightarrow lo \uparrow$... does not work!



 

PR: $\bar{x} \wedge \bar{lo} \wedge \bar{ro} \wedge \bar{ri} \wedge \bar{li} \rightarrow lo \uparrow$

For lo...

 


CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [ri]]$

PR: $\bar{x} \wedge \bar{lo} \wedge \bar{ro} \wedge \bar{ri} \wedge \bar{li} \rightarrow lo \uparrow$



$\bar{x} \wedge \bar{ri} \rightarrow lo \uparrow$

For lo...

 

CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [ri]]$


PR: $\bar{x} \wedge \bar{lo} \wedge \bar{ro} \wedge \bar{ri} \wedge \bar{li} \rightarrow lo \uparrow$



$\bar{x} \wedge \bar{ri} \rightarrow lo \uparrow$

$x \vee ri \rightarrow lo \downarrow$

For lo...

 



CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [r\bar{i}]]$

PR: $\bar{x} \wedge \bar{lo} \wedge \bar{ro} \wedge \bar{ri} \wedge \bar{li} \rightarrow lo \uparrow$




$\bar{x} \wedge \bar{ri} \rightarrow lo \uparrow$


$x \vee ri \rightarrow lo \downarrow$

  


For $ro \dots$

 

 CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]]$




For x...

 

CHP: * $[lo \uparrow]$ $[li]$; $x \uparrow$; $lo \downarrow$; $[\bar{li}]$; $[ro \uparrow]$ $[ri]$; $x \downarrow$; $ro \downarrow$; $[\bar{ri}]$

The CHP sequence is annotated with red and blue circles and arrows. The first three terms, $[lo \uparrow]$, $[li]$, and $x \uparrow$, are enclosed in red circles. The last three terms, $[ro \uparrow]$, $[ri]$, and $x \downarrow$, are enclosed in blue circles. A black arrow points upwards from below the $x \uparrow$ term. Another black arrow points upwards from below the $x \downarrow$ term.


For $x \dots$

 

CHP: $* [lo \uparrow] [li]; x \uparrow; lo \downarrow; [\bar{li}]; [ro \uparrow] [ri]; x \downarrow; ro \downarrow; [\bar{ri}]$

... What gate is this?

For $x \dots$

 


CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]]$

The CHP sequence is shown with red circles around $[li]$, $x \uparrow$, and $[\bar{ri}]$, and blue circles around $[\bar{li}]$, $[ri]$, and $x \downarrow$. Two black arrows point upwards to the $x \uparrow$ and $x \downarrow$ terms.


PR: $\bar{ri} \wedge li \rightarrow x \uparrow$

$ri \wedge \bar{li} \rightarrow x \downarrow$


For $x \dots$

 

 CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]]$




Putting it together

 


CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]$

Circuit:

 


Mind wires...

 


CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]]$

Circuit:

 


Mind forks...

 


CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]]$

Circuit:

 


Checking fork "li" (1)

 


CHP: $*[lo \uparrow] [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [r\bar{i}]$

Circuit:

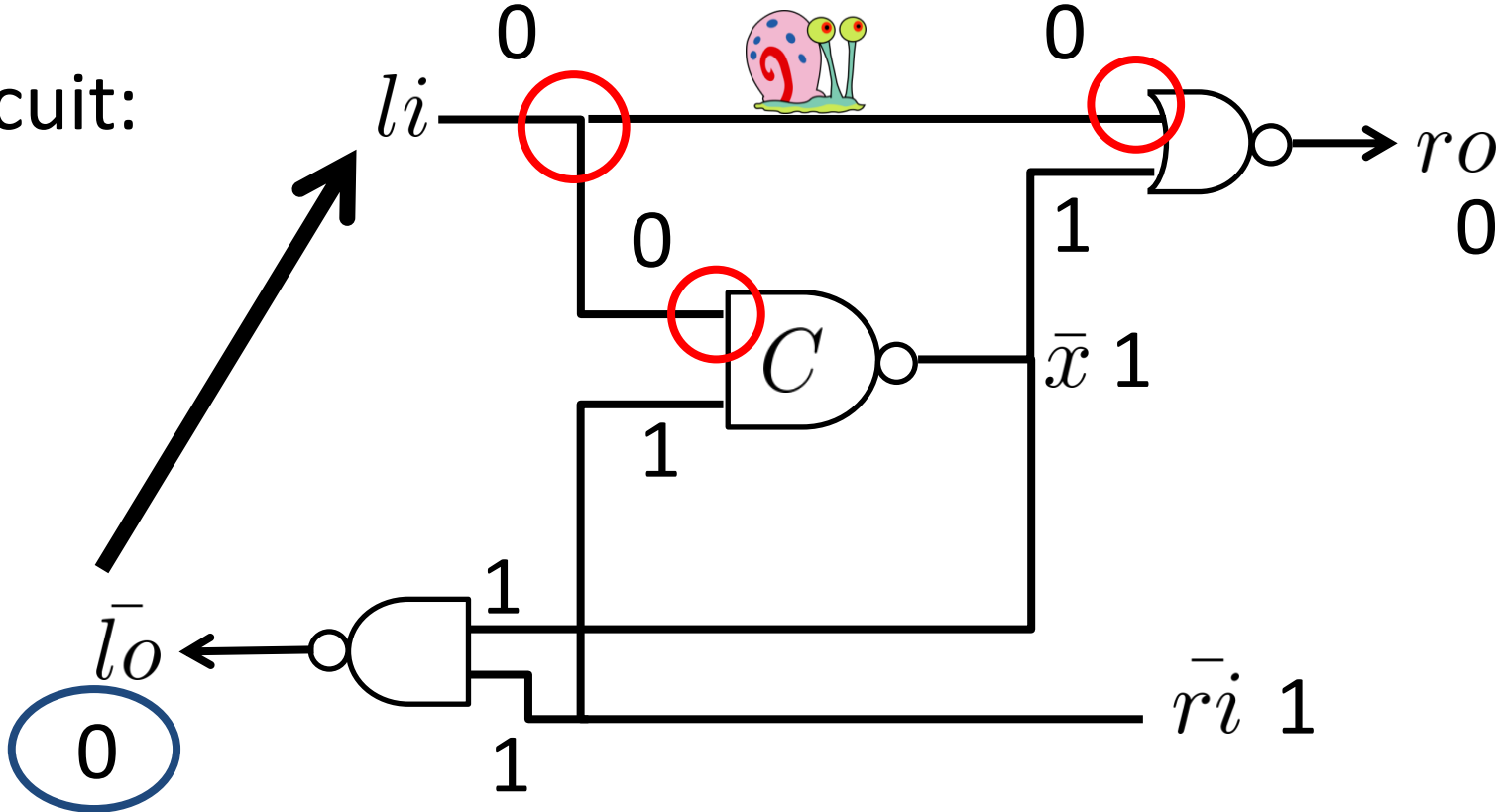


Checking fork "li" (1)

 


CHP: $*[lo \uparrow] [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [r\bar{i}]$

Circuit:

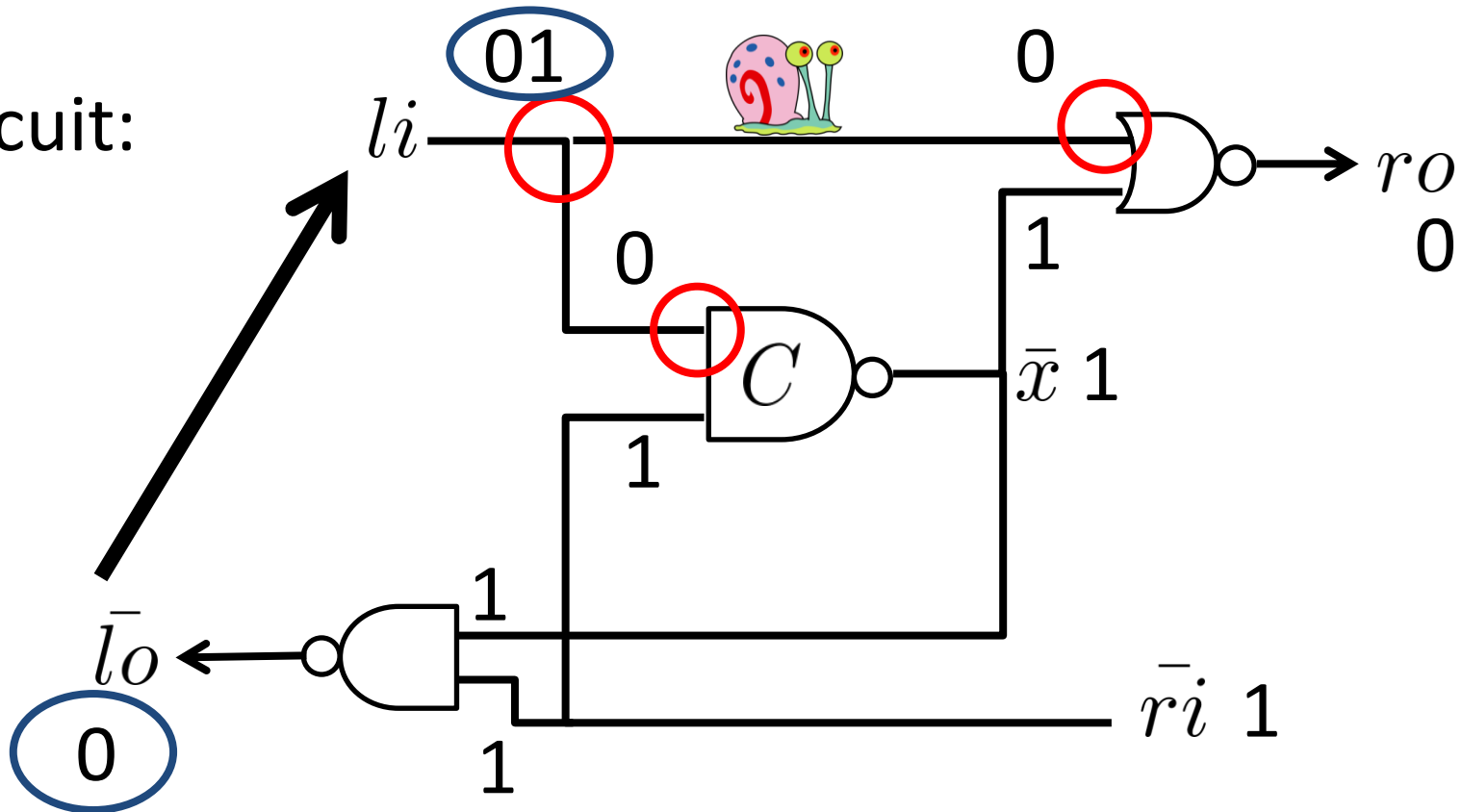


Checking fork "li" (1)

 


CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [r\bar{i}]]$

Circuit:

 


Checking fork "li" (1)

 


CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [r\bar{i}]]$

Circuit:

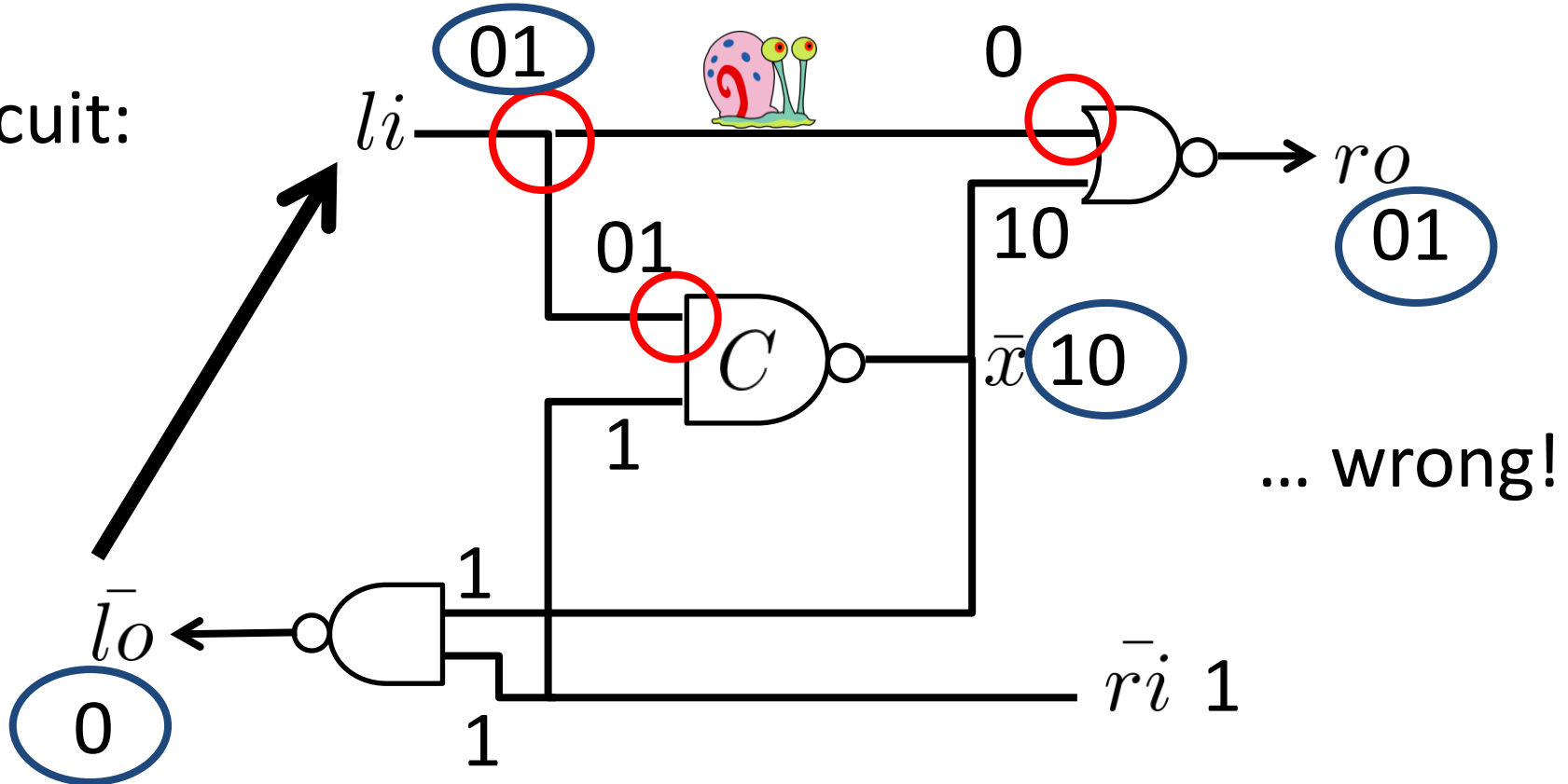


+ one-sided Constraint

 


CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]$

Circuit:

 

+ one-sided Constraint

 


CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]]$

Proving correct:

e.g. by induction.

base case: start with initial states and prove ordering of events from there for the first loop

+ one-sided Constraint

 

CHP: $*[lo \uparrow] [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]$

proof:


examine ordering in time “<”.

1) **lo-up < [li]**: guaranteed by environment:

Initially $li = 0$. Can be set to $li = 1$ only by

environment. Environment does this only after $lo = 1$.

+ one-sided Constraint

 


CHP: $*[lo \uparrow; [li] \cdot x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]]$

proof:

2) $[li] < \mathbf{x-up}$: $x = 1$ can happen only after both C-Element inputs are 1. This can happen only after $li = 1$ for the first time.

+ one-sided Constraint

 

CHP: $*[lo \uparrow; [li]; x \uparrow; lo \downarrow; [\bar{li}]; ro \uparrow; [ri]; x \downarrow; ro \downarrow; [\bar{ri}]]$

proof:

3) **x-up < lo-down**: this can happen only if one of the NAND inputs becomes 0 for the first time.

We first show that lo-down cannot happen because of the input connected to not ri becoming 0:

[hw project]

Hw project

- Prove: PR circuit implements CHP circuit:
all executions generated by PR circuit fulfil
CHP properties.
- Use: NuSMV
model checker
see e.g. nusmv.fbk.eu/NuSMV/tutorial


Hw project

- Input:
 - automaton specification (PRs) + fairness condition
 - Linear Temporal Logic (LTL) formula to verify
- Output:
 - formula holds vs. does not hold + counterexample

active -> passive

active L, active R,


CHP: $P1 : *[L; R]$

 



→

passive L, active R,



CHP:

 

4ph-hs active -> passive

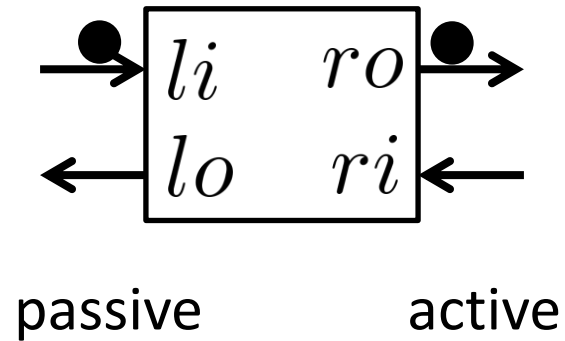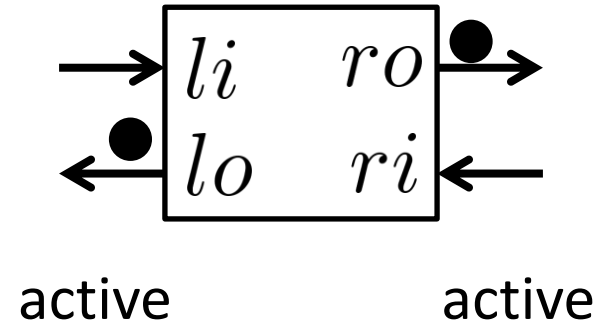

4ph-hs active -> passive

  

[hw]

Beyond classical circuit design

lecture 6.5

Gate internals

Further Reading

Simon M. Sze, Kwok K. Ng: *Physics of Semiconductor Devices*. 3rd edition. Wiley, 2006.

Jan M. Rabaey, Anantha Chandrakasan, Borivoje Nikolic: *Digital Integrated Circuits. A Design Perspective*. 2nd edition. Prentice Hall, 2003.

Why look inside?

- Why is stability important?
 - > Runts/metastability
- What if it does not hold?
 - > Dealing with them.
- Optimization for speed/power/size/robustness...

In principle...

Schrödinger equation in space and time

$$i\hbar \frac{\partial}{\partial t} \psi(x, t) = H\psi(x, t)$$


in one dimension

$$i\hbar \frac{\partial}{\partial t} \psi(x, t) = -\frac{\hbar^2}{2m} \frac{\partial^2}{\partial x^2} \psi(x, t) + V(x, t)\psi(x, t)$$

In principle...


assuming steady state

$$\psi(x, t) = e^{i\omega t} \psi(x)$$

 

In principle...

 
simplified model: single e- in periodic potential



Carriers

e^- electron


$\mathcal{E} \longrightarrow$

 

Carriers

e^- electron

$\mathcal{E} \longrightarrow$

 

Carriers

e^- electron

h^+ hole

$\mathcal{E} \longrightarrow$

