

# Beyond classical circuit design

## lecture 9

### Alternative Design Styles

# Further Reading


Jan M. Rabaey, Anantha Chandrakasan, Borivoje Nikolic: *Digital Integrated Circuits. A Design Perspective. 2<sup>nd</sup> edition*. Prentice Hall, 2003.

# Remember: CMOS Design

Combinational Logic:

n-stack: down transition  $G \rightarrow y \downarrow$

 p-stack: up transition  $\neg G \rightarrow y \uparrow$




# Ratioed-logic: Pull-up

Combinational Logic

$$G \rightarrow y \downarrow$$


$$\neg G \rightarrow y \uparrow$$

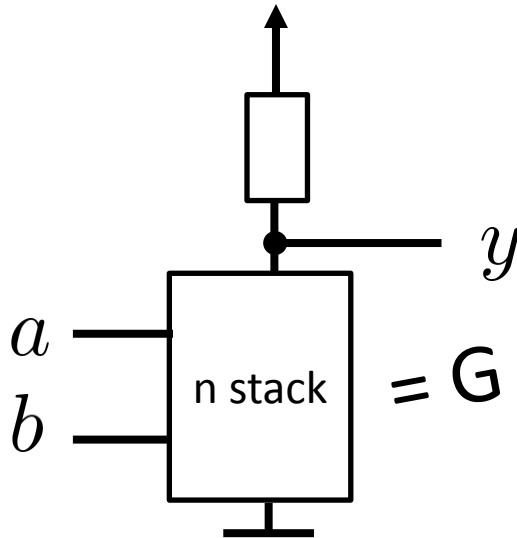


Circuit size?

Static power?


# Pseudo-NMOS

 

# Pseudo-NMOS NOR

 


versus

 

# Pass-transistor Logic

AND gate

 


Mind: reduced voltage swing!

# Pass-transistor Logic

In general:


... what about this wrt. voltage swing?

 




# Pass-transistor Logic

Complete pass gate

 

versus

 

[Hw]


# Beyond classical circuit design

## lecture 9.5


### Clocked Design Styles

# Latch


Positive latch

 

Negative latch

 


Positive latch behavior

 

# Positive Latch Implementation



by transmission gates

 


# Positive Latch Implementation

by transmission gates

But mind:

  


versus

 

# Positive Latch Implementation


by transmission gates

 

What is the load signal  $E$  has to drive?



# Positive Latch Implementation

by NMOS pass transistors

 



What is the load signal  $E$  has to drive?

# Flip-flop: edge triggered

 
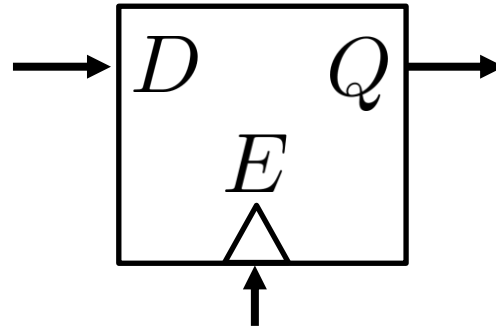





# Flip-flop: edge triggered

  


# Flip-flop: positive edge triggered

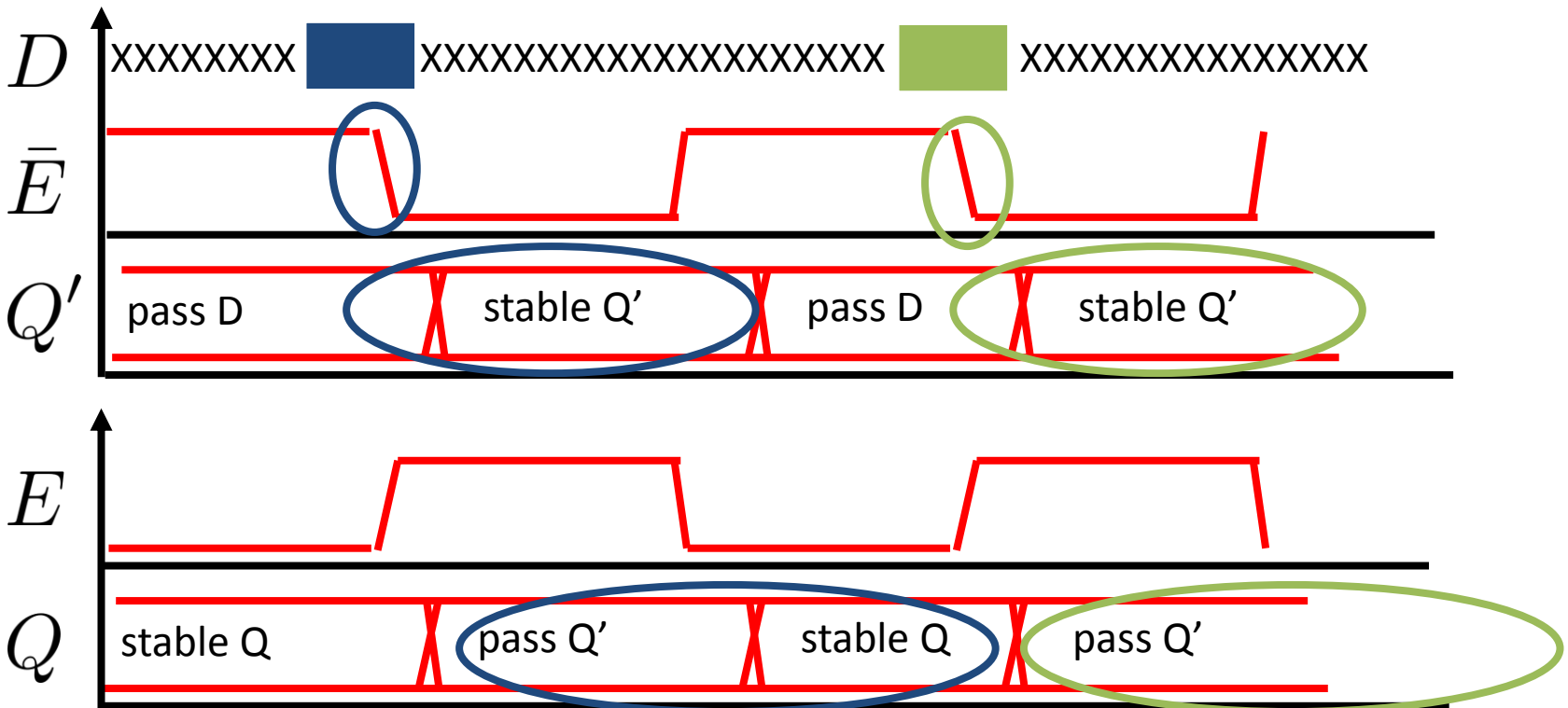 



# Reducing E-load

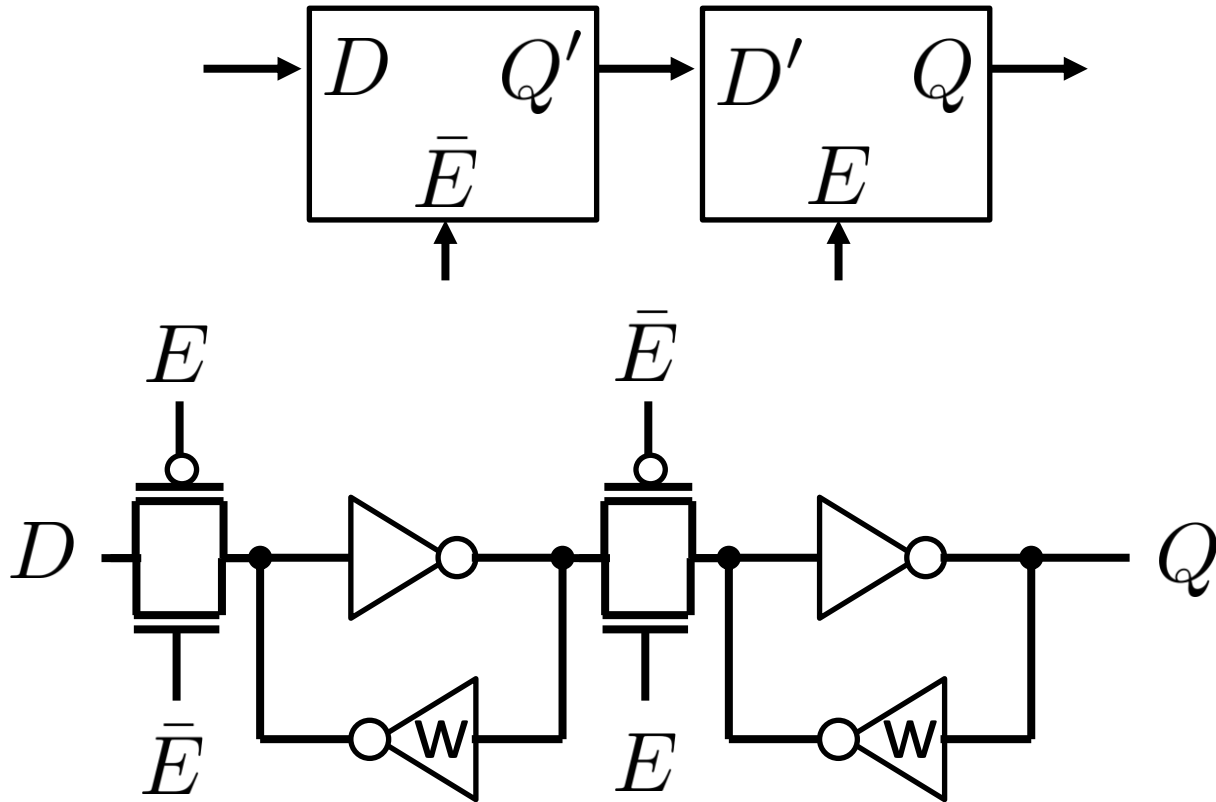


# Mind sizing

 


# Preventing this...

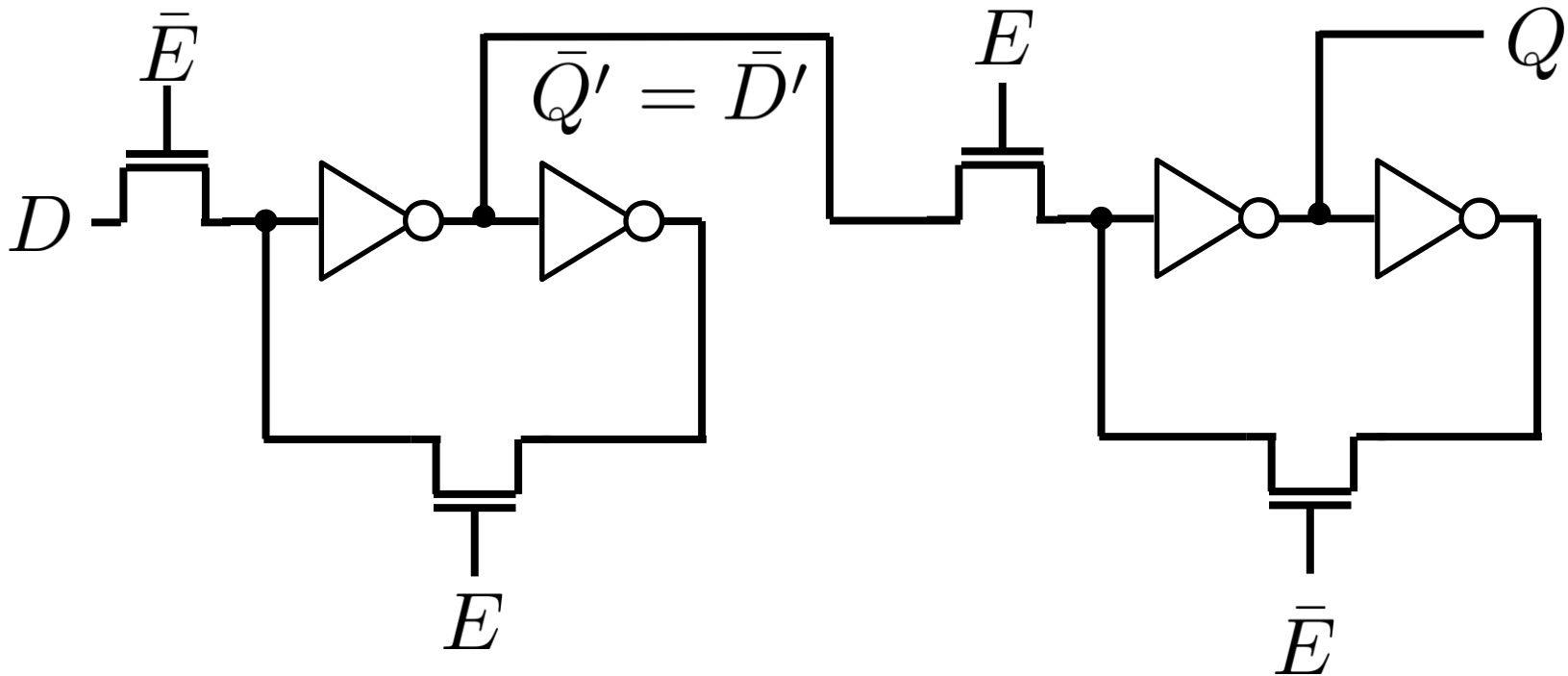 


# Mind phases

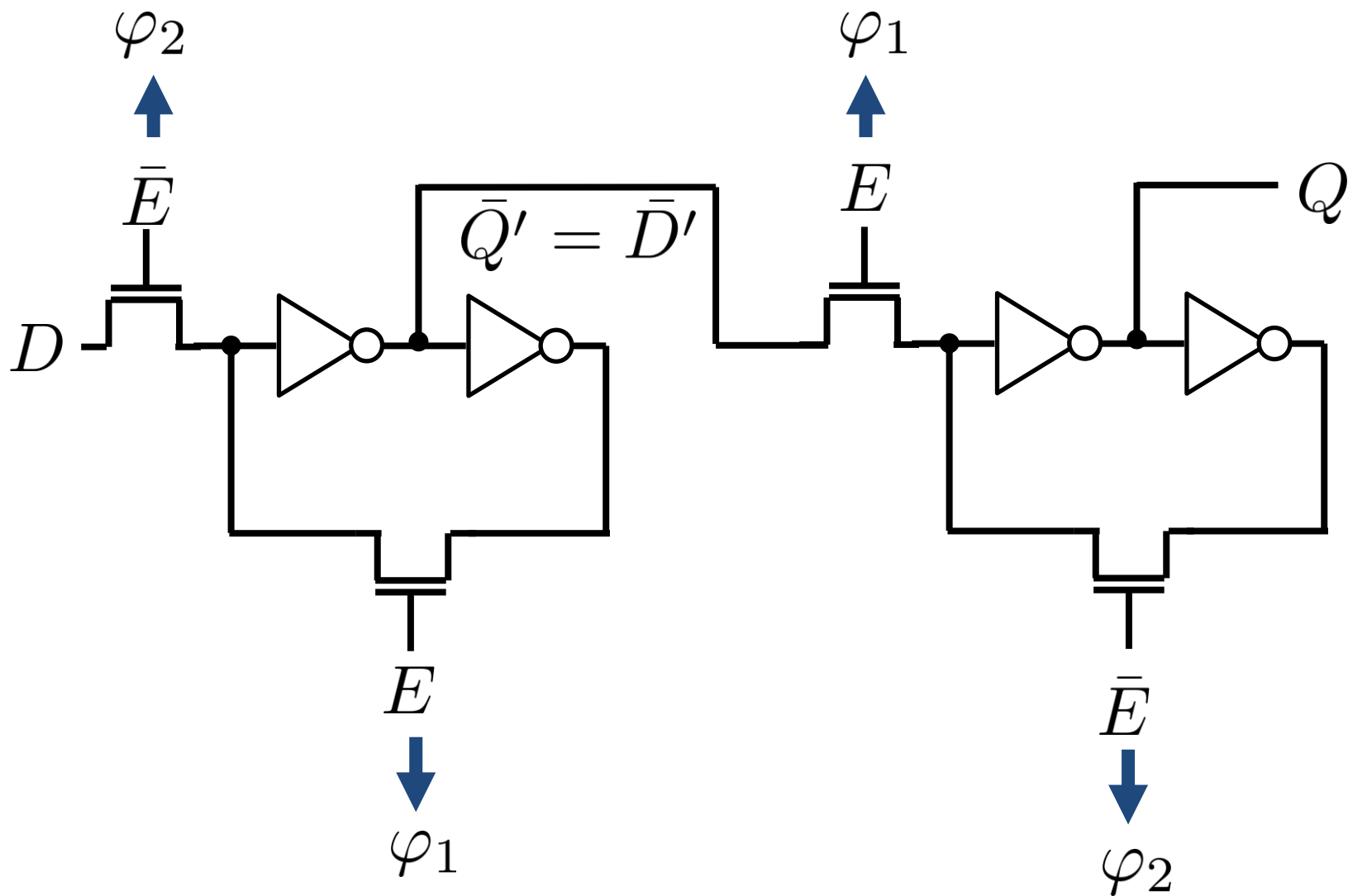

# Mind phases

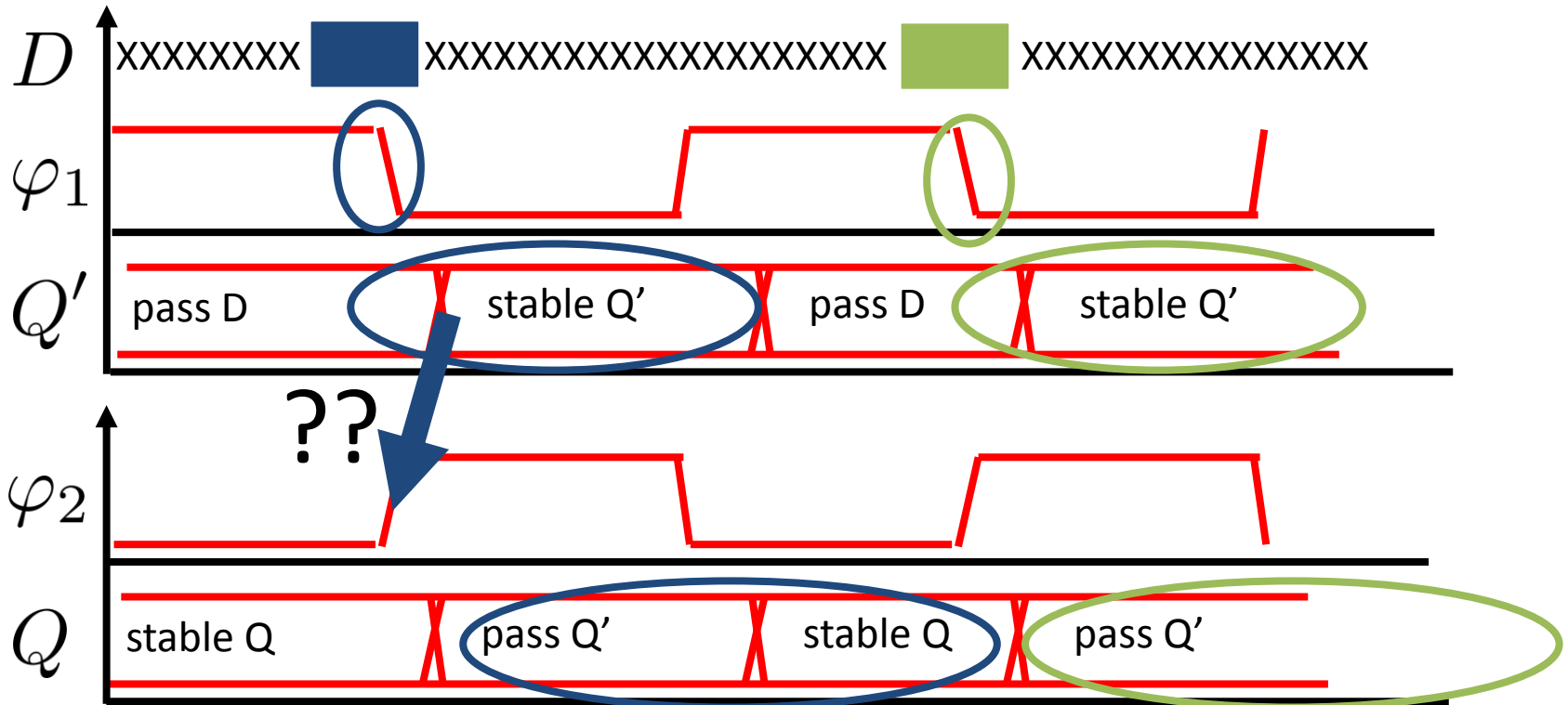


# Mind phases

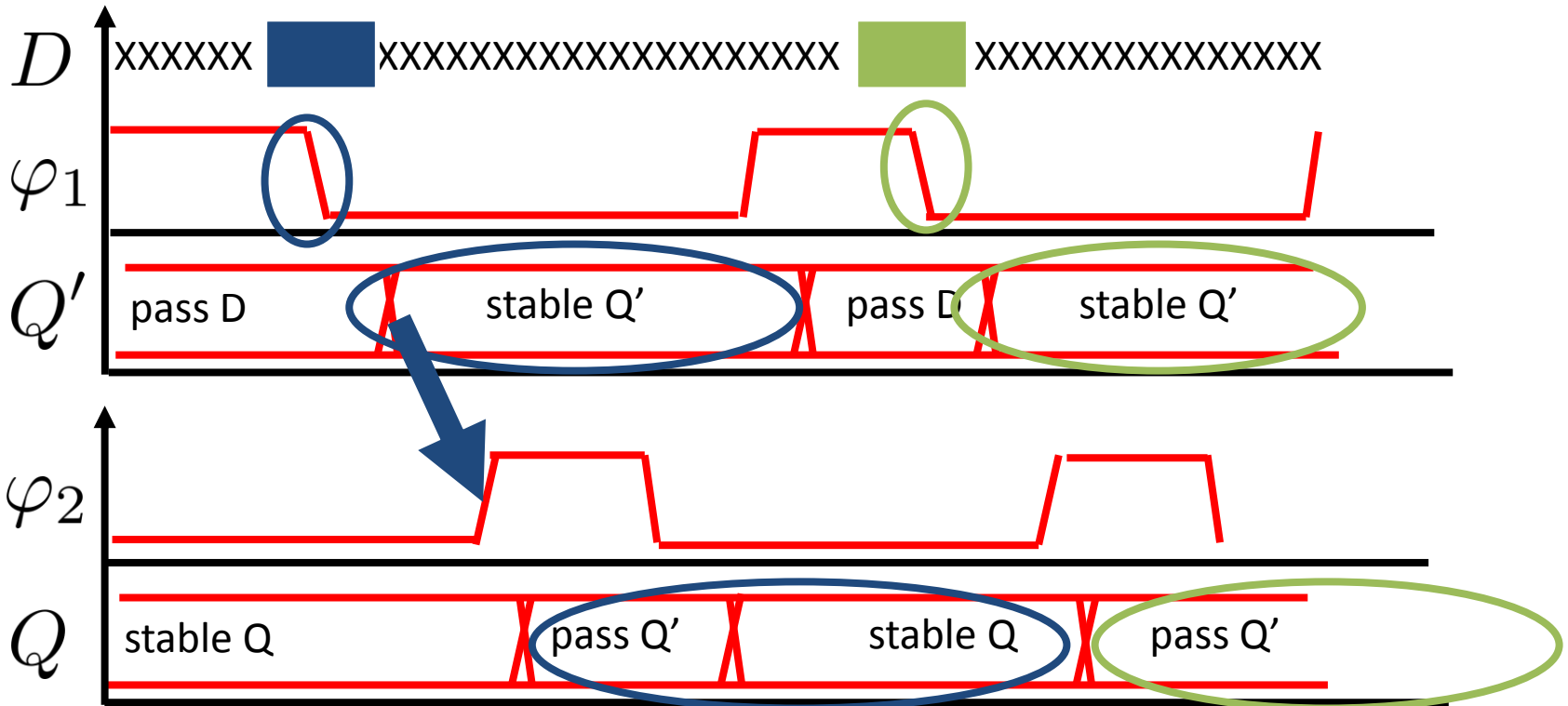





# Generate phases (locally)

 



locally since otherwise:

- two signals to distribute
- non-overlap problem, again



# Generate phases (locally)

  



# Generate phases (locally)

  



# Generate phases (locally)

  

# Generate phases (locally)

  

# Generate phases (locally)

  

# Is this static?

