

Beyond classical circuit design
lecture 9

Alternative Design Styles

Further Reading


Jan M. Rabaey, Anantha Chandrakasan, Borivoje Nikolic: *Digital Integrated Circuits. A Design Perspective. 2nd edition*. Prentice Hall, 2003.

Remember: CMOS Design

Combinational Logic:


n-stack: down transition $G \rightarrow y \downarrow$

 p-stack: up transition $\neg G \rightarrow y \uparrow$



Ratioed-logic: Pull-up

 
Combinational Logic $G \rightarrow y \downarrow$
 $\neg G \rightarrow y \uparrow$



Circuit size?
Static power?

pull-up instead of p-stack

Pseudo-NMOS

 

implementation with MOSFETs

thus the name "ratioed": the pMOS acting as a pull-up resistor must not be too strong compared to the pull-down nMOS


that is: the ratio W/L of pMOS and W/L of nMOS must fulfill a certain ratio for the circuit to work correctly.

Pseudo-NMOS NOR



Pass-transistor Logic

AND gate

 


Mind: reduced voltage swing!

Pass-transistor Logic


In general:

... what about this wrt. voltage swing?

 


Pass-transistor Logic

Complete pass gate

 

versus

 


[Hw]

Beyond classical circuit design
lecture 9.5


Clocked Design Styles

Latch


Positive latch

 

Negative latch

 


Positive latch behavior

 

negative latch specified analogously with inverted enable signal E_{-}


Positive Latch Implementation

by transmission gates

 


Positive Latch Implementation

by transmission gates

 

But mind:

 


versus

Assumes a perfectly inverted signal $\bar{E} = \text{not } E$.

Positive Latch Implementation

by transmission gates

 


What is the load signal E has to drive?

E and \bar{E} drive 4 transistors.

Positive Latch Implementation


by NMOS pass transistors

 

What is the load
signal E has to drive?

Using Q instead of \bar{Q} increases the load for the pass gate. Decoupling it by an INV is often a better choice to get a fast storage loop.
 E and \bar{E} drive 2 transistors.

Flip-flop: edge triggered

 


positive edge triggered flip-flop:

on positive transition of $E \rightarrow$ copy stable D to output Q and hold until next change.

assumption: D is stable around positive edge of E (before edge: setup time, after edge: hold time).


If not: either copy arbitrary value to output, or even become metastable (discussed later on)

Flip-flop: edge triggered

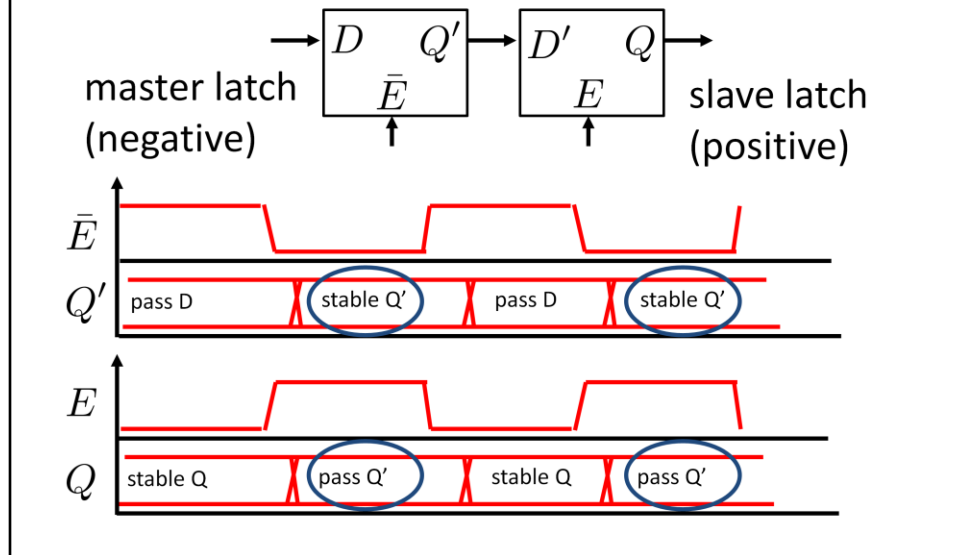


whenever slave passes, master is stable.

Flip-flop: positive edge triggered

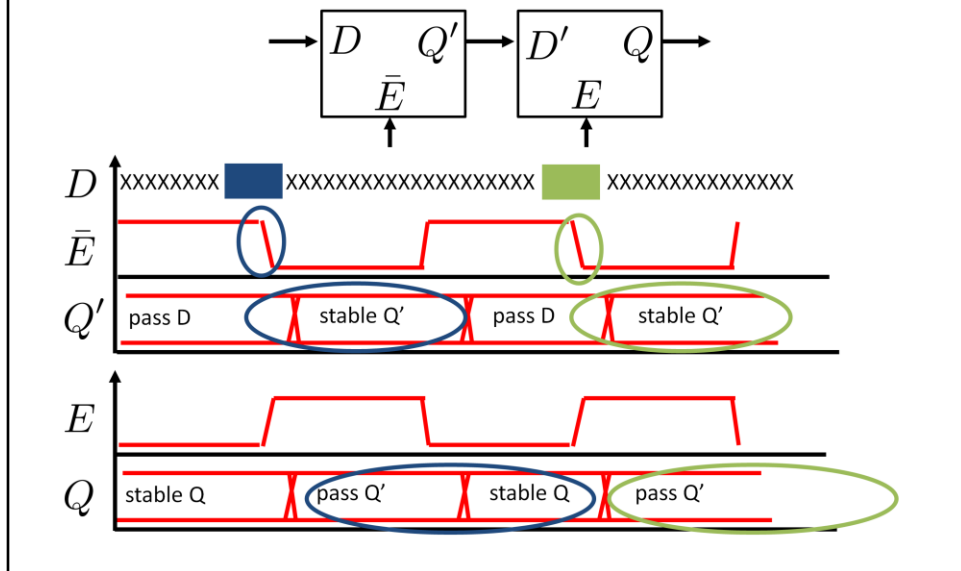


blue & green: data waves that are stable values.

Reducing E-load

 

by removing the feedback-loop pass gates, we reduce size and load signals E and \bar{E} have to drive


Mind sizing

 


removing the feedback -> attention has to be paid that the slave could influence the master.

However, weak INV drives against INV.

Preventing this...

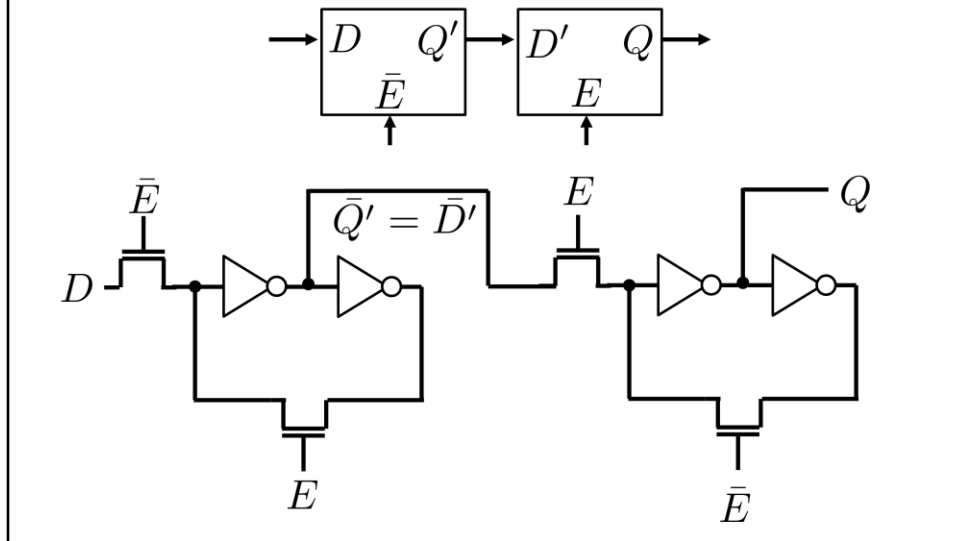


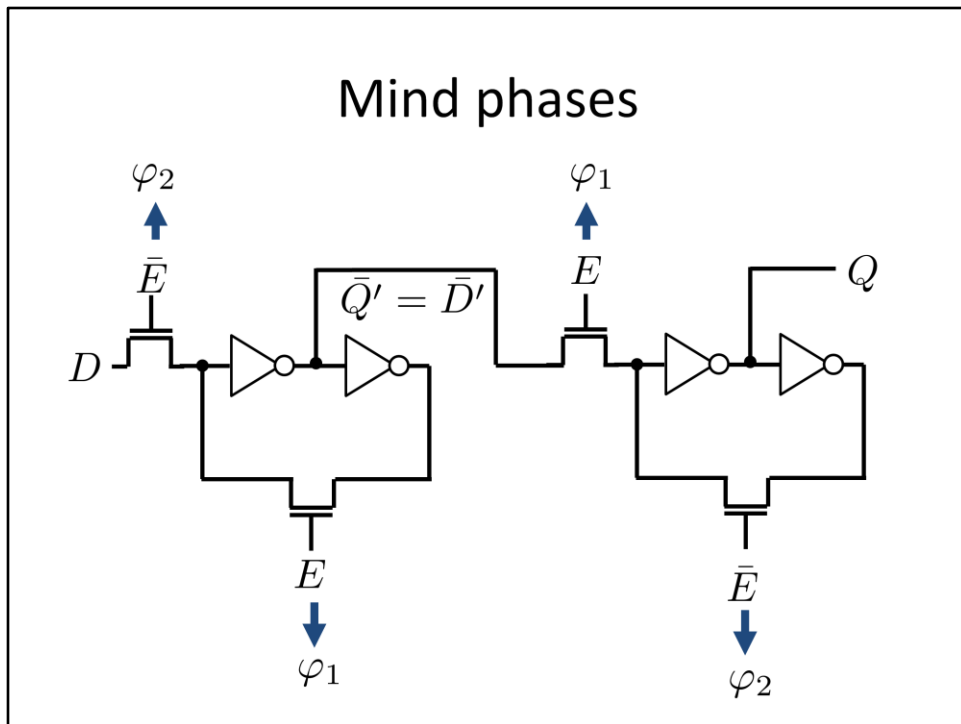We would like to prevent this (driving against each other). But, do not want to increase load -> use the nMOS pass transistor implementation from before.




instead of E and \bar{E} use two aligned phases φ_1 and φ_2 .
 Here: just renaming and decoupling from E .

Mind phases

 


possible timing violation

Mind phases

 

clearly separated phase signals φ_1 and φ_2 .

Generate phases (locally)

 


locally since otherwise:

- two signals to distribute
- non-overlap problem, again



from Rabaey et al. Digital Integrated Circuits (2nd ed) p339

Generate phases (locally)

 


initial steady state

Generate phases (locally)

  

... still unstable

Generate phases (locally)


 


... stable state after E had a positive transition.

Note the “happened before” constraints for both E -up \rightarrow φ_1 up and φ_2 down \rightarrow φ_1 up.



This guarantees well-separating between φ_1 and φ_2 .

Generate phases (locally)

  


... still not stable

Generate phases (locally)

  

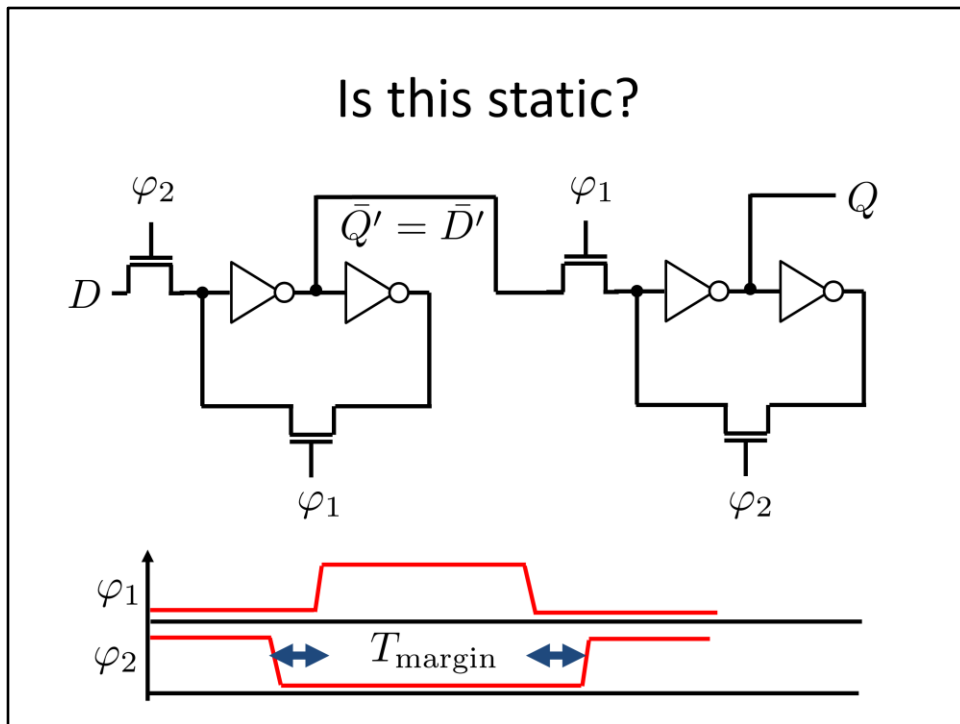stable again. From here on cyclic behavior.
Mind the well-separated phases.



higher T_{margin} -> better separation between phases and thus less chance of overlap due to e.g. delay variations

However: comes at a price (not only performance): implicit (wire/load) capacitance has to hold charge in the meantime -> decharging might be harmful if T_{margin} is too long.